

Roll No. ....

**300111****December, 2019**

**B. TECH. 1st SEMESTER (UNDER CBS)  
BASIC ELECTRICAL ENGINEERING (ESC-101)**

Time : 3 Hours]

[Max. Marks : 75

- Note: 1. It is compulsory to answer the questions of Part-A.  
Limit your answers within 30-50 word in this part.*
- 2. Answer any four questions from Part-B in detail.*
- 3. Different parts of the same question are to be attempted adjacent to each other.*

**PART - A**

1. (a) A 50 W resistance is connected across a 10 V battery. What is the current through the resistor? Find the energy consumed in 8 s. (1.5)
- (b) The resistance of two wires is 25 W when connected in series and 6 W when joined in parallel. Calculate the resistance of each wire. (1.5)
- (c) An alternating current is represented by  $i = 12 \sin 314 t$ . Find out (a) Frequency (b) Instantaneous Value at  $t = 4 \text{ ms}$  (c) Time taken to attain a value of 10 A for first time after passing through zero. (1.5)

- (d) Define duality. What is the dual of capacitance and resistance? (1.5)
- (e) A balanced star-connected load of  $(3-4j) \Omega$  is connected to 400 V supply. What is the real power consumed by the load? (1.5)
- (f) Draw and explain equivalent circuit of auto transformer. (1.5)
- (g) Write the principle of operation of DC generator. (1.5)
- (h) Differentiate between buck and boost converter. (1.5)
- (i) Differentiate between MCB and MCCB. (1.5)
- (j) Write down the various characteristics of batteries. (1.5)

### PART - B

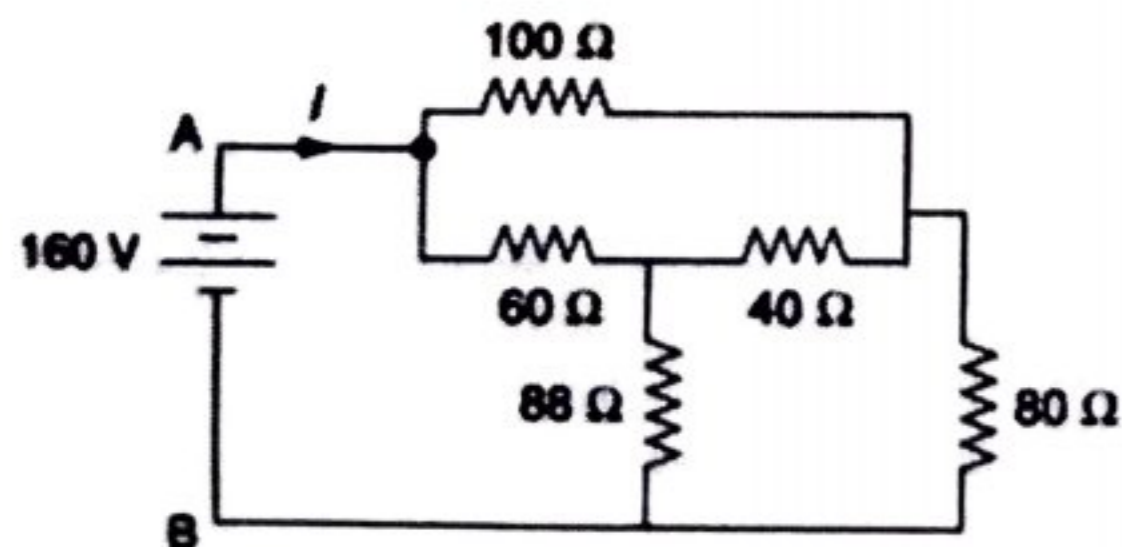


Figure 1(a)


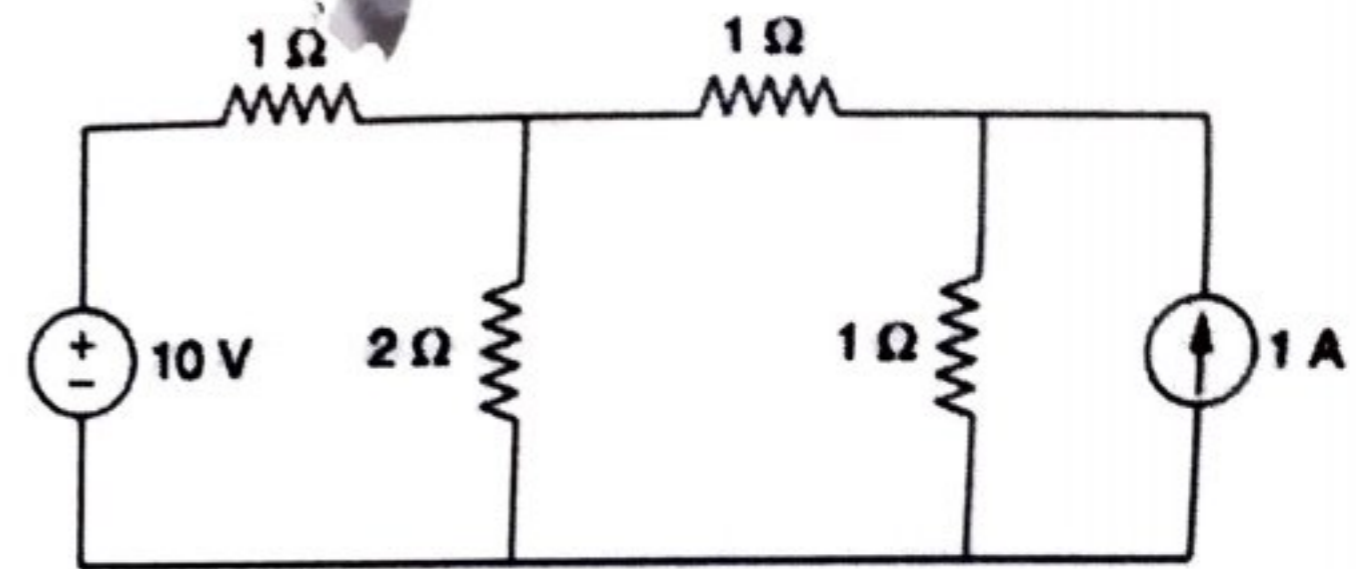


Figure 1(b)

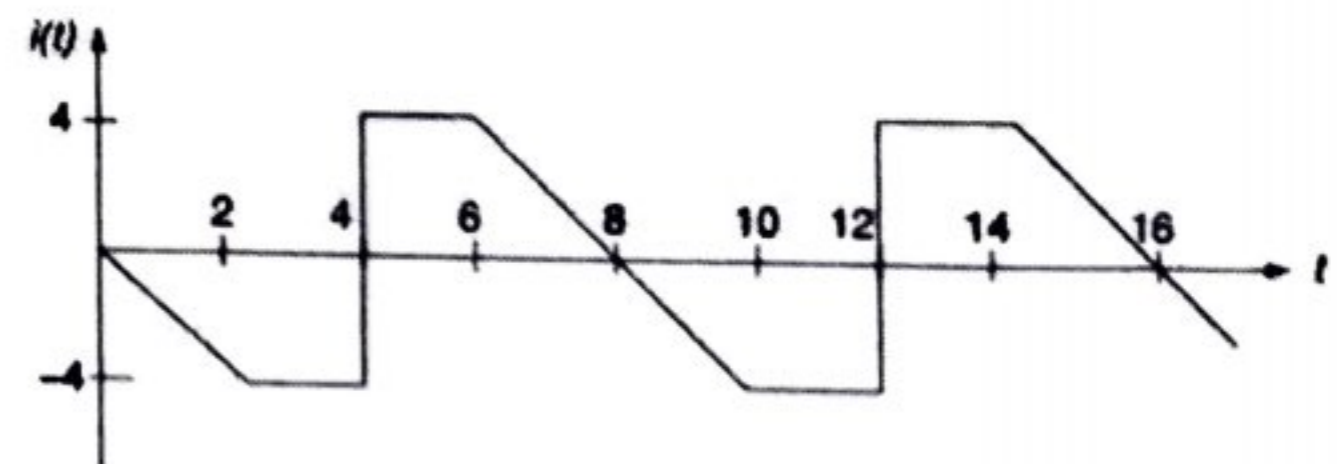- (a) Determine the current  $I$  in the Figure 1(a). (7.5)
- (b) Calculate the current through the  $2\Omega$  resistor in the circuit shown in Figure 1(b), using superposition theorem. (7.5)
3. (a) Find the RMS and Average Value of current wave form shown in figure below : (7.5)



- (b) Derive the expression for power factor measurement by using two wattmeter method. Also discuss the various case related to it. (7.5)

4. (a) What is a B–H curve? Explain the hysteresis and eddy current loss. How are they minimized? (7.5)
- (b) Describe efficiency and regulation of single phase transformer with various equations related to them. (7.5)
5. (a) Explain the different types of rotor in three phase induction motor. (7.5)
- (b) What do you mean by synchronous motor? Differentiate synchronous motor from induction motor. (7.5)
6. Write a short note on single phase and three phase voltage source inverter in brief. (15)
7. (a) What do you mean by Earthing? Explain its various types in brief. (7.5)
- (b) Define the term power factor. Write down the various benefits of power factor improvement. (7.5)
-