

Roll No. ...22021002023

Total Pages : 4

002202

July 2023

B.Tech. - II SEMESTER

Basic Electrical Technology (ESC-101-A)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) What is the significance of form factor and peak factor? (1.5)
- (b) What is the purpose of using laminated core in a transformer? (1.5)
- (c) State the Superposition theorem. (1.5)
- (d) Distinguish between active circuit and passive circuit. (1.5)
- (e) Define the voltage regulation of transformer. (1.5)


002202/1165/111/5

397 [P.T.O.

- (f) What is the difference between dependent source and independent sources? (1.5)
- (g) How do you make Single-Phase Induction Motor Self-Starting? (1.5)
- (h) How Back Emf is generated in a DC motor? What is the significance of back emf? (1.5)
- (i) What are the advantages of three-phase system over single-phase system? (1.5)
- (j) Explain the difference of fuse and MCB. (1.5)

PART-B

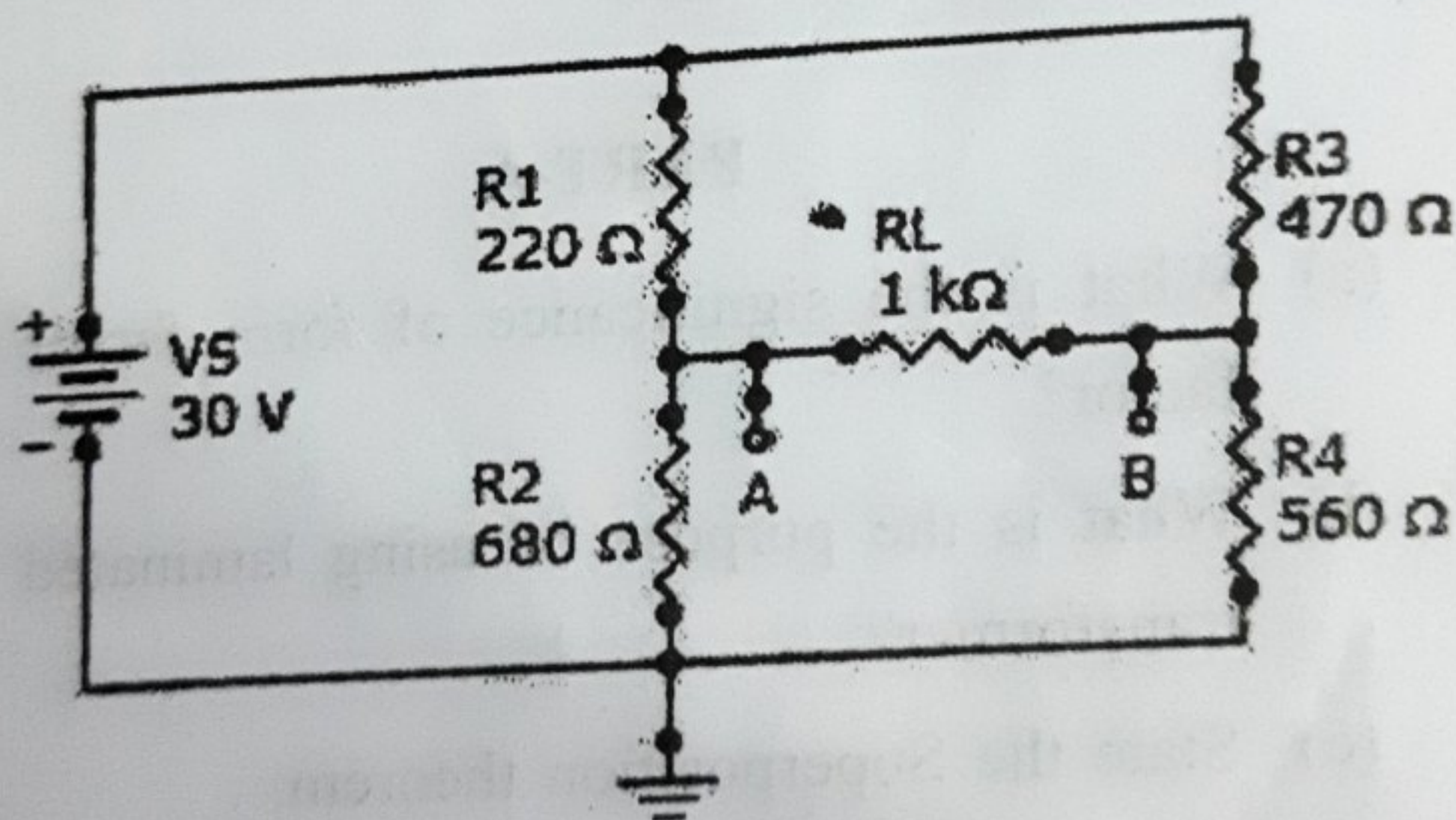2. (a) Find the Thevenin equivalent (V_{TH} and R_{TH}) between terminals A and B of the circuit given below. (7.5)



- (b) A balanced three phase load consists of three coils each having resistance of 4 Ω and inductance 0.02 H. It is connected to a 415 V, 50 Hz, 3-phase ac supply. Determine the phase voltage, phase current,