

Analog to Digital Converter


An analog to digital Converter takes an analog input V_a as input and generates a digital output D where $D \propto V_a$

⇒ Process

If the input signal is sinusoidal i.e., changes at every instant of time during conversion, final value D may be erroneous. So during the conversion we can use a sample and hold circuit to sample the input voltage and hold it to a constant value.

Sample and hold circuit ^{consist} of a switch and a capacitor and two voltage followers op amp.

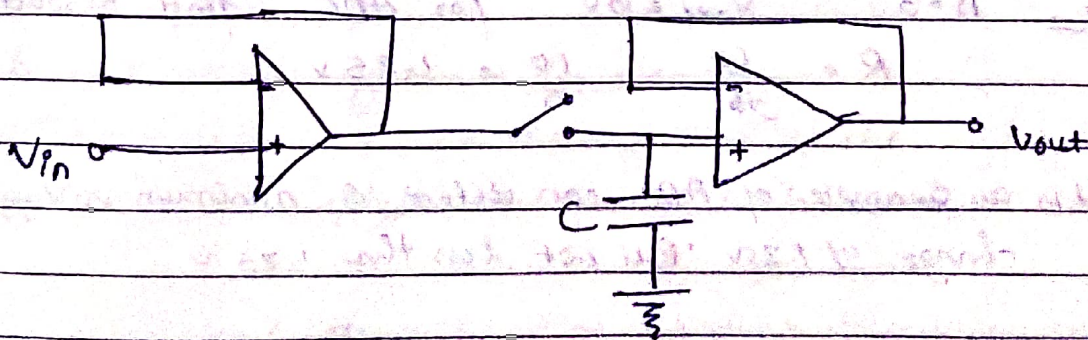
When the switch is closed the capacitor charges upto input voltage V_{in} and when the switch is opened the capacitor holds that voltage until the switch is closed again. Thus output voltage remains reasonably constant.



Sample & Hold Circuit

Quantization

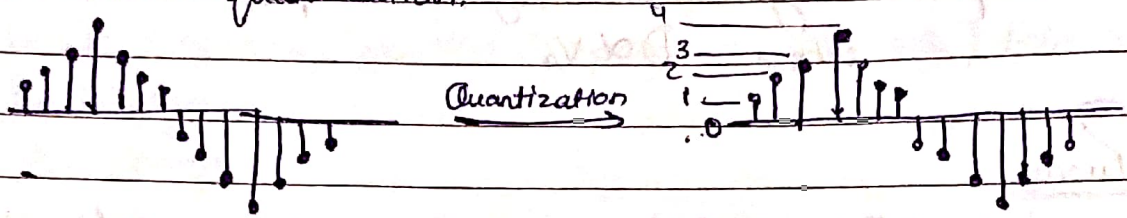The process of assigning a sample signal and value for the discrete set of values be nearest possible integer is called quantization.



Here we introduce a term called "resolution" which represents how much the quantised value is close to the actual value. It is generally defined in terms of number of bits.

Thus "Resolution" defines the minimum change in the input signal that can be detected.

$$\text{Resolution} = \frac{\text{Full scale range}}{2^{\text{(no. of bit)}}} = \frac{V_{\text{max}} - V_{\text{in}}}{2^n} = \frac{V_{\text{ref}}}{2^n}$$

where $n =$ ~~bit~~ no. of bits

$2^n =$ No. of discrete levels of quantization

Ex $n = 3$ $V_{\text{ref}} = 10\text{V}$ for ADC find Resolution


$$R = \frac{10}{2^3} = \frac{10}{8} = 1.25\text{V}$$

it is an Example of ADC can detect a minimum voltage change of 1.25v. But not less than 1.25v

* To increase resolution increase the no. of bit and decrease the full scale range (V_{ref})

Encoding: The last process of ADC is encoding in which the quantised values are converted into digital binary numbers i.e. in the form of 0s & 1s.

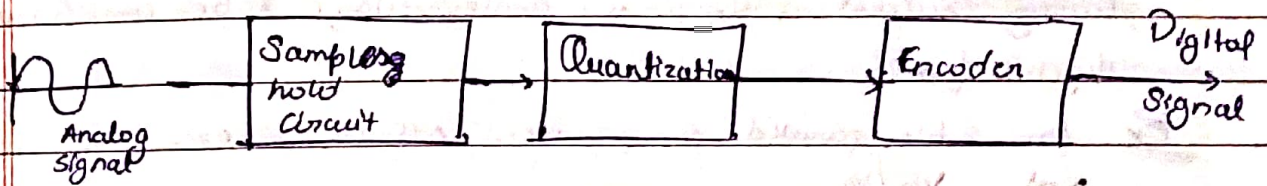Thus the whole process of Conversion of an analog to Digital may be expressed as.



Specification of A/D Converter


- # Conversion time \rightarrow of an ADC is the time required by ADC to perform a complete conversion process. The conversion is commonly started by sample clock.
- # Accuracy \rightarrow of a converter refers to how many bits from conversion to conversion are repeatable. That is accuracy reflects how the ADC outputs reflects the actual input.
- # Integral non linearity error (INL) - Offset and gain error, and the accuracy of the voltage reference, temperature effect and AC performance.
- # Sensitivity \rightarrow describes the smallest absolute amount of change that can be detected by a measurement of often expressed in terms of millivolts, microvolts.

The easiest way to determine the sensitivity of a device is to look at its performance on its lowest range.

Flash / Parallel ~~ADC~~ Comparator (ADC)

It is formed of a series of comparators, each one comparing the input signal to the unique reference voltage. The comparators outputs connect to the input of a priority encoder ckt. which then produces a binary output. V_a is the analog voltage to be converted into digital form.

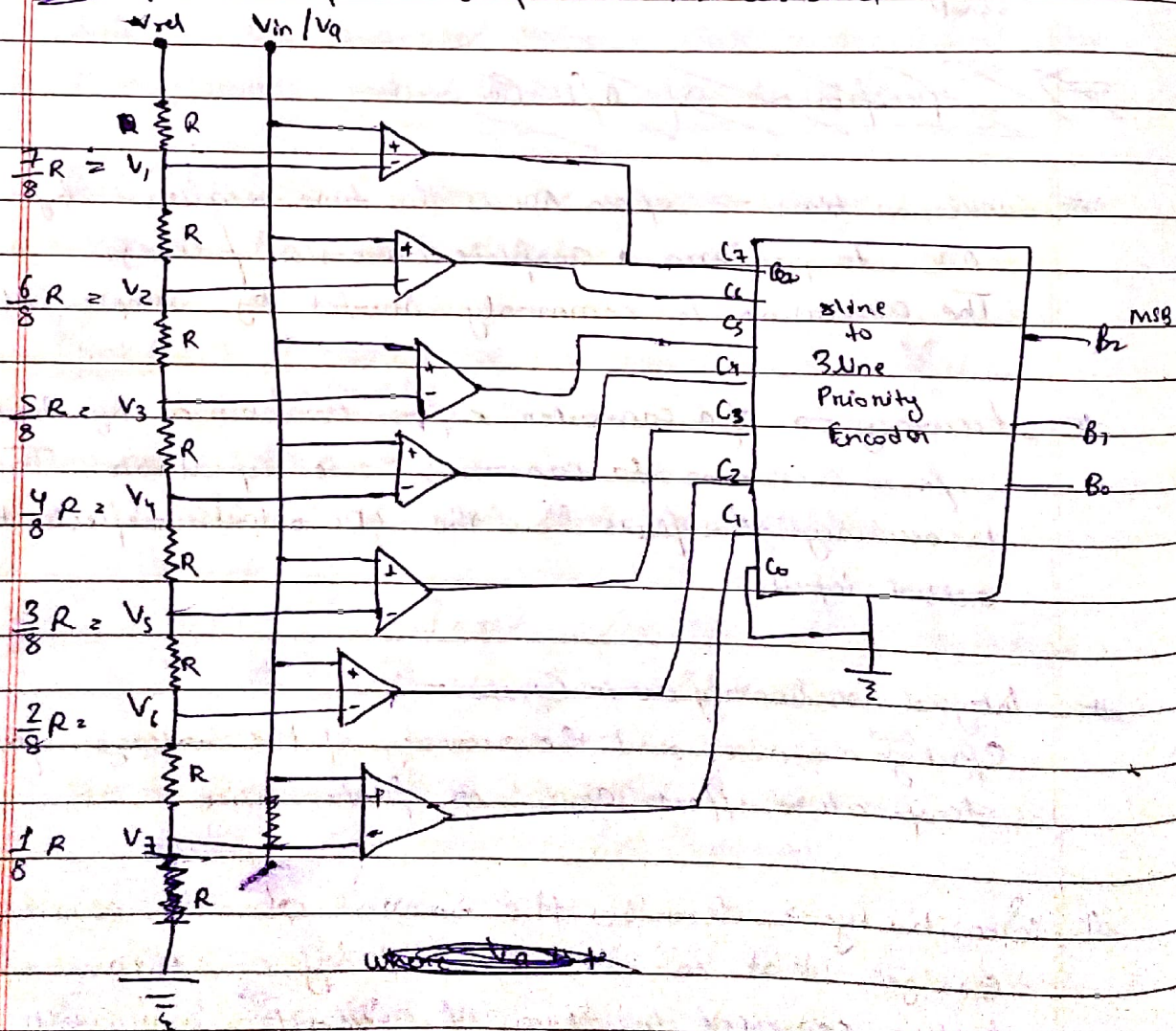Ex for 3 bit parallel comparator ADC Converter



Advantages

- Low cost
- Low sensitivity to noise and temp change
- Simple and fast procedure
- Good conversion accuracy, only one clock required

Disadvantage

- Rapid increase in the no. of comparators ~~with the no.~~ with the no. of bits ($2^n - 1$ comparators are required for an n bit converter)
- Costly and more resistor is used

⇒ 3 bit flash type ADC

No. of comparator is used $2^n - 1 = 7$

Input of encoder = $2^n = 8$

No. of resistor = $2^n = 8$


Encoder — $2^n : 3 \Rightarrow 8 : 3$

V_{in} at non inverting terminal

V_{ref} at inverting terminal

If $V_{in} \geq V_{ref} = 1$


If $V_{in} < V_{ref} = 0$

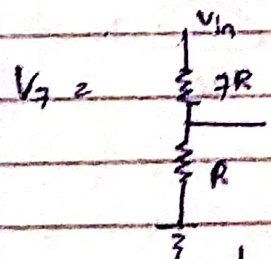

$V_7 =$

$V_7 = \frac{V_{ref} \times 7R}{7R + R}$


$\frac{V_{ref}}{8} = \frac{V}{8}$

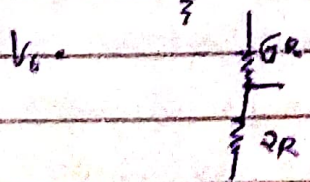

$V_6 =$

$V_6 = \frac{V_{ref} \times 2R}{6R}$

$= \frac{2V}{8R} = \frac{1}{4} V$

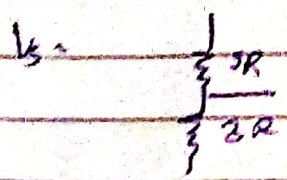


$V_5 =$

$V_5 = \frac{V_{ref} \times 3R}{5R}$


$= \frac{3V}{8}$

Successive- Approximation A/D Converter

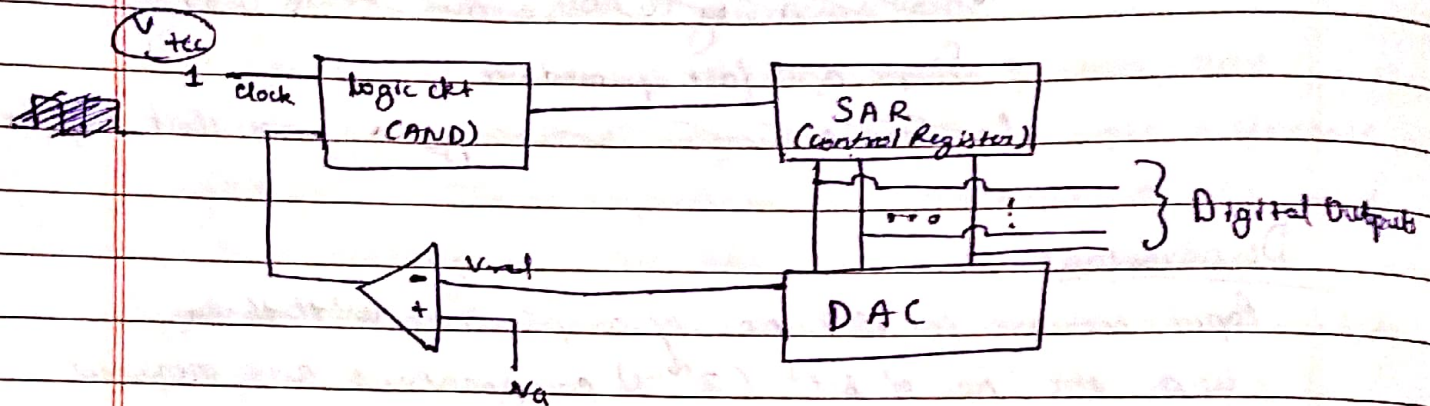

- If $V_a > V_{ref} = \text{high (1)}$ case 1
- $V_a \leq V_{ref} = \text{low (0)}$ case 2

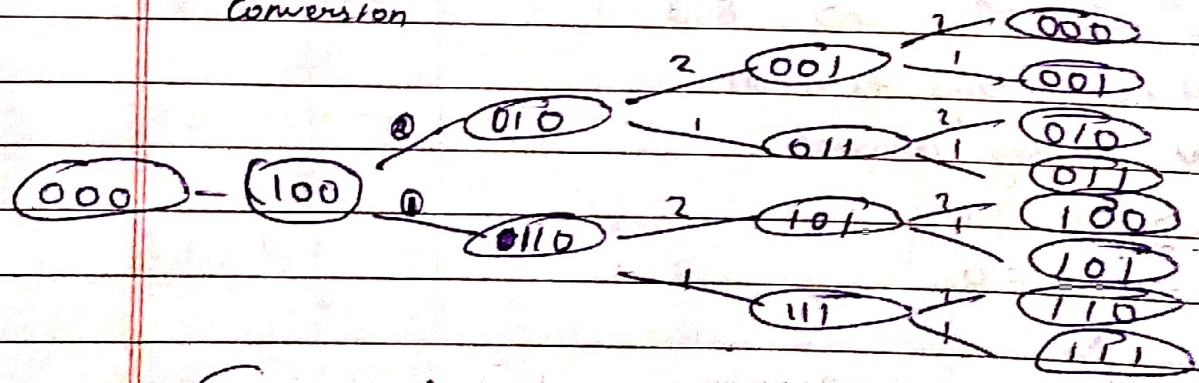A successive Approximation A/D is a type of analog to Digital Converter that convert a continuous analog waveform into a discrete digital representation using a binary search through all possible quantization levels before finally converging upon a digital output for each conversion.



Conversion time = ~~2^n Tclk~~ $n Tclk$
 = $3 Tclk$


$T = (2^n - 1) Tclk$

- Advantages
- Faster than Counter type ADC Converter
 - Not effected by amplitude of input voltage
 - Low power consumption

- Disadvantages
- Ckt is complex in comparison to counter type
 - low ~~of~~ speed (slow) than flash type ~~ADC~~ ADC

Working - If V_{in} is greater than the output of ~~comparator~~ the DAC (V_{ref}) the most significant bit will stay as it is and the next bit will be set for a new comparison otherwise if the V_{in} is less than DAC value the MSB will set to zero and next bit set to 1 for a new comparison.

Counter type ADC

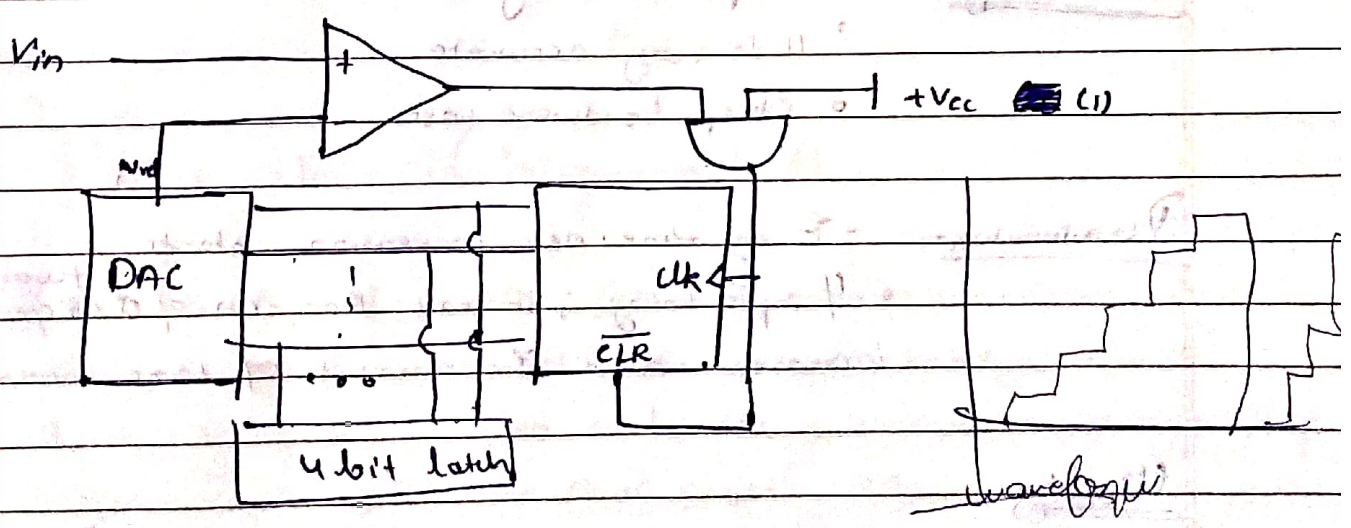

Counter type ADC produces a digital output which is approx equal to analog input by using counter operation internally.

- Comparator used in two open loop configuration than it can be used as comparator
 If V_{in} greater than V_{ref} V_{in} at non inverting terminal
 V_{ref} at inverting terminal \Rightarrow the output of comparator is high
- Clock generator - generates the clock pulse
- Control logic - ~~logic gate~~ ^{here} ~~works~~ work as a clock generator
~~and~~ are used to reset the counter and enable the clock signal
 and send to the counter
- latch - used to store the output of counter
- DAC - converts the received ~~an~~ digital input and converts into an analog signal

Advantages

- Simple and easy to use
- It is very accurate
- Cheap hardware cost

Disadvantages

- Every time new conversion starts
- If input voltage is increase than no. of ~~bits~~ ^{turns} increases and the amount of time increases

Working

During the start of conversion the output of DAC is zero so whether input voltage V_{in} is applied at the +ve terminal of comparator the output of comparator is high

Since it is high the AND gate is enable and it allow clock pulse to pass. The counter then start counting the clock pulse. The output of counter is feed to the DAC which converts the decimal equivalent of its binary input. Now the output of DAC is in form of staircase. Now compare with the input V_{in}

As long as $V_{in} > V_{ref}$ the counter keep counting. If $V_{in} < V_{ref}$ the output of comparator is low then and gate is disable and clock is 0 therefore counting will stop and #


Conversion time is defined as the time taken by it to convert a given analog to digital signal

$$= (2^n - 1) T_c$$

Double slope (Integrating) ADC

In Double slope type ADC the integrator generates two different ramps, one with the known analog input voltage V_A and another with a reference voltage $-V_{ref}$. Hence it is called as dual slope ADC.

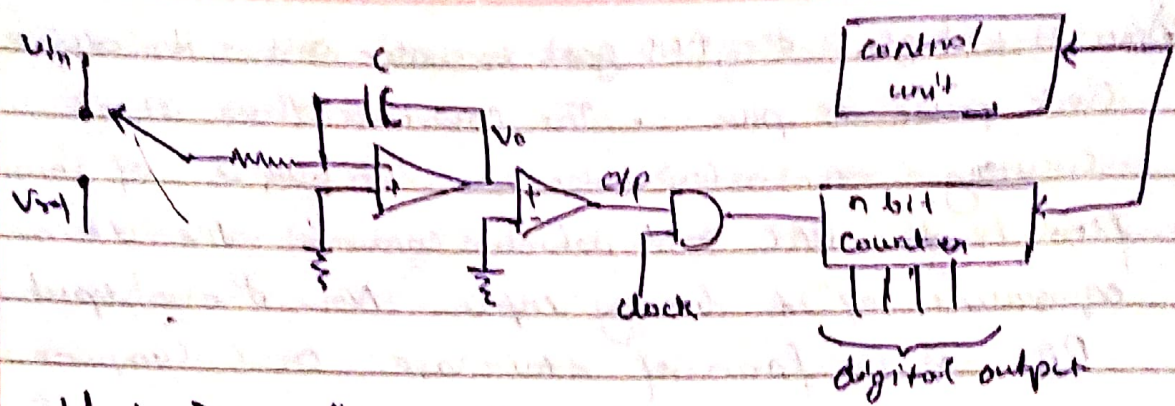In this method one voltage is ~~two~~ in inverse polarity. If V_{in} is +ve then V_{ref} is -ve and vice versa.




If $V_o > 0$ Voltage level 1
 If $V_o < 0$ Voltage level 0

It is consist of Reference voltage, comparator, integrator, binary counter

$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt = -\frac{V_{in}}{RC} [t]$$

Let $V_{in} = V_a$

$$V_o = -\frac{V_a t}{RC}$$

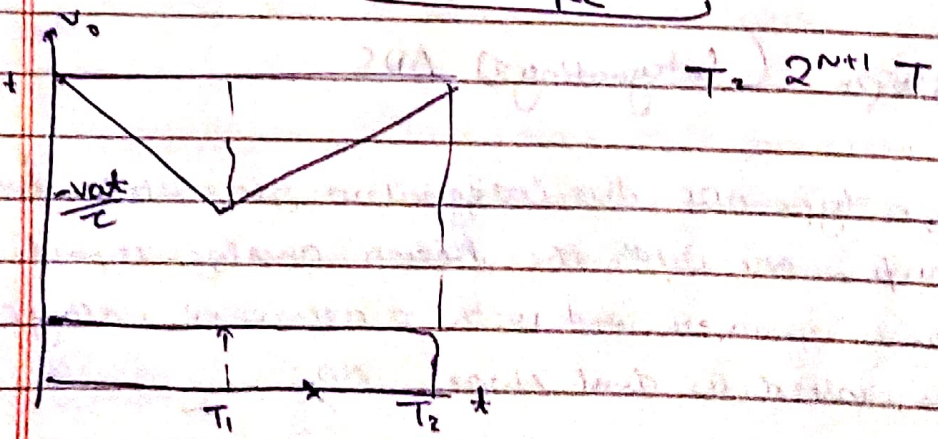

Advantage • Accuracy Good • Low cost • Low sensitivity to noise

Disadvantage • ~~slow~~ ^{this} process the slowest conversion time

Specification ADC

- 1) Range of Input Voltage
- 2) Input Impedance
- 3) Accuracy
- 4) Conversion time
- 5) Format of Digital Output

Examples of IC

ADC 0801

ADC 0802

ADC 0803

ADC 0804

ADC 080

Common used
range 0-5V
8bit