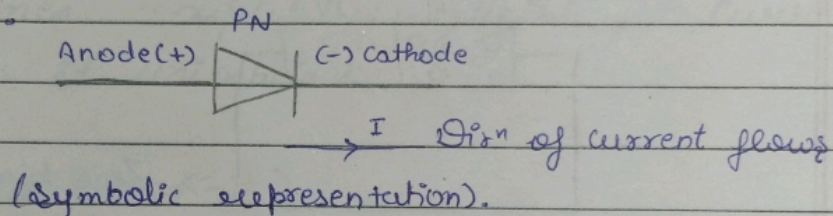


Module-1

1. PN junction Diode →

- P-N junction diode is also known as semiconductor diode.
- When a p-type semiconductor is joined to n-type semiconductor, the contact surface is called p-n junction.
- It is two-terminal device that conducts current only in one direction.



• Formation of P-N junction diode →

We use diff. s/c materials to make a P-N junction there will be a boundary that inhibit the movement of e^- from one side to another side, by scattering the e^- and holes,

Thus we use the process of doping, if we add a part of the p-type silicon will get converted to N-type silicon. This side sheet will contain both the P & N-Type region & a junction of b/w these two regions.

The process that follows after forming a p-n junction are of two types i) Diffusion
ii) Drift.


Date: / /
Page No.

3 Biasing Condition for P-N junction diode →

There are three biasing condition for P-N junction diode.


- (i) Zero biasing (I $\otimes$)
- (ii) Forward Bias (++, --)
- (iii) Reverse Bias (+-, -+)

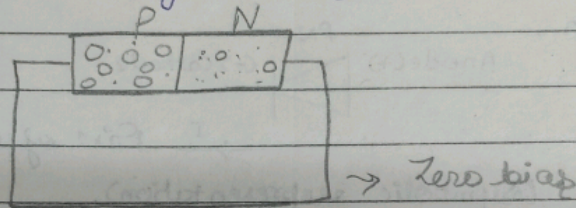(i) Zero Biasing → when no external voltage is applied to the P-N junction diode,
→ There is no flow of current.



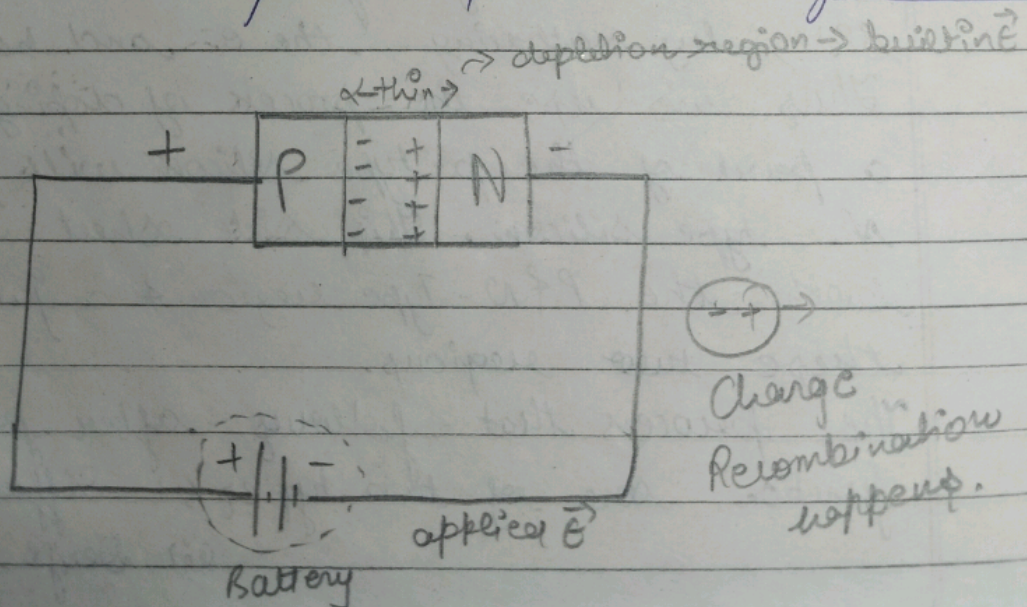(ii) Forward biasing → (++, --)

when the P-type is connected to the battery's (+) terminal and the N-type is connected to the (-) terminal, then the P-N junction is said to be forward Bias.




When the P-N junction is forward biased the built in electric field at the P-N junction & the applied electric field are in opp. dirⁿ. When both the e.f. add up, the resultant electric field has a mag. lesser than the built in electric field. This results in less sensitive and thinner depletion region.

- The Depletion Region's resistance becomes negligible when the applied voltage is large.
- In Silicon, At 0.6V the resistance of the depletion region becomes completely negligible & current flows across it unimpeded.

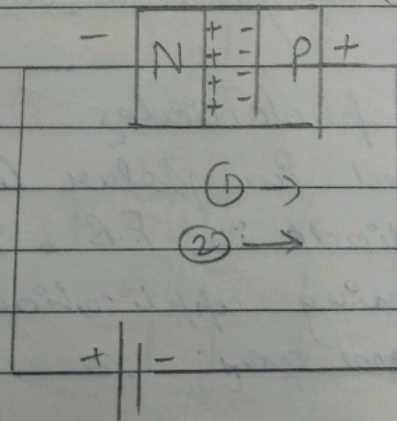(iii) Reverse bias $\rightarrow (+, -)$

- When the p-type is connected to the battery's (-) terminal & the N-type is connected to the (+) side, this is called P-N junction reverse bias.
(No current flows).




- (1) $\rightarrow$ built in e.f.
- (2) $\rightarrow$ battery induced e.f.

- The built-in e.f. and the applied e.f. are in the same dirⁿ.
- Depletion region becomes more sensitive & thicker if the applied voltage becomes larger.

* V-I Characteristics of P-N junction diode →

It is a curve b/w the V and I through the circuit.

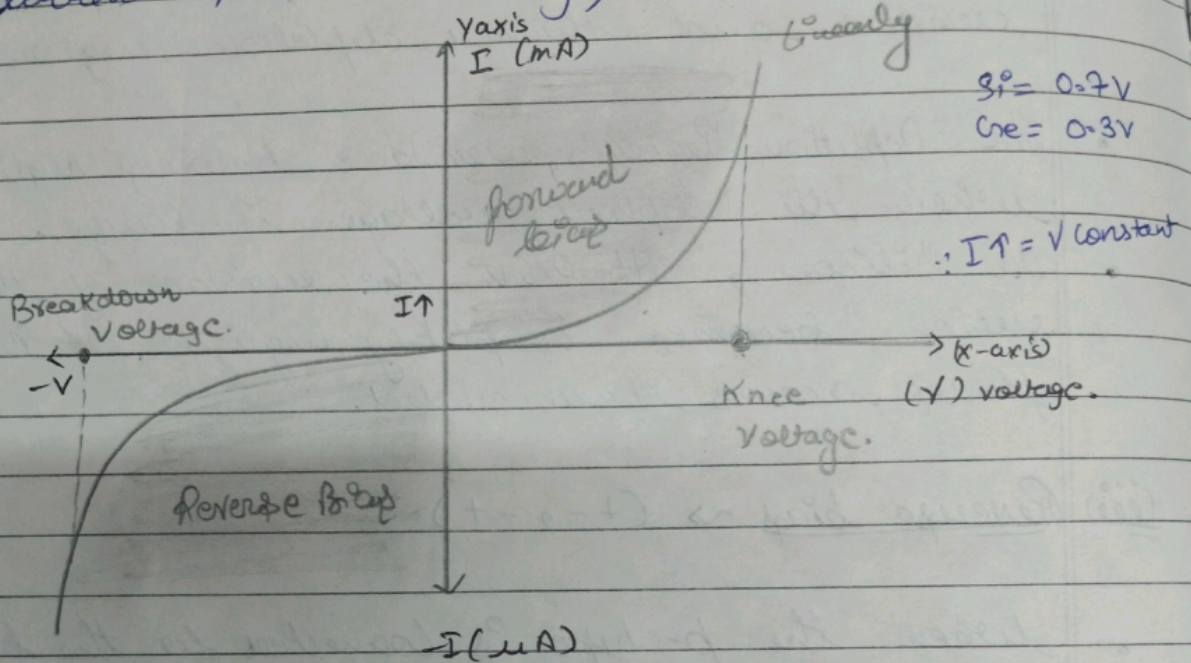voltage is taken along x-axis while the current is taken along y-axis.



☞ Application of P-N junction diode →

- It is used as photodiodes
- It can be used in solar cells.
- When the diode is F.B. It can be used in LED lighting application.
- They also used as a voltage controlled oscillator


★ Rectifier → A rectifier is a device which converts an AC input voltage into a DC output voltage.

• Principle → A rectifier's principle is to convert AC to direct current (DC) by allowing current to flow in one dirⁿ, while restricting it in other. This process is called rectification.

• P-N junction diode can be used either as
(a) half wave rectifier
(b) full wave rectifier.

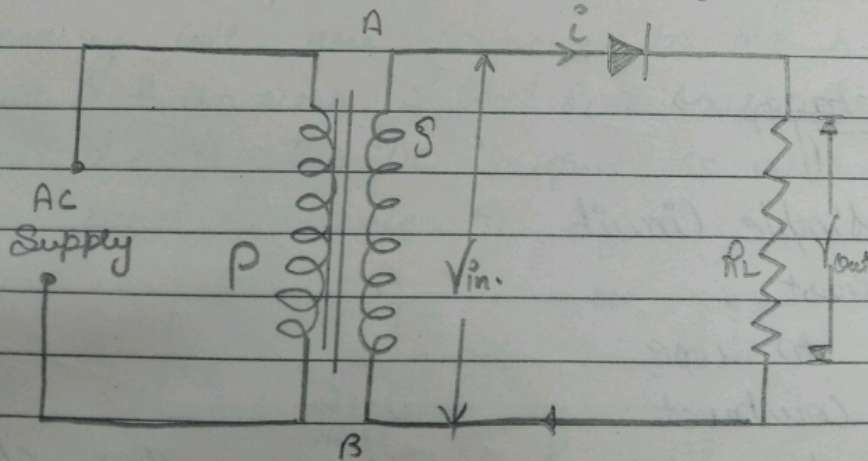(a) Half wave rectifier →


Construction → • The AC - input voltage is fed across the primary coil P. of a step-down trans.
• The Secondary coil S. of trans. connected with S/c p-n junction diode D and a load resistance R_L .



Working → • During 1st half cycle → of AC input the end A be at +ve potential & end B at -ve potential in Secondary S of trans. In this Diode is F.B & current flows in circ. & An Output voltage across load R_L obtained.

◦ During 2nd half of AC input →

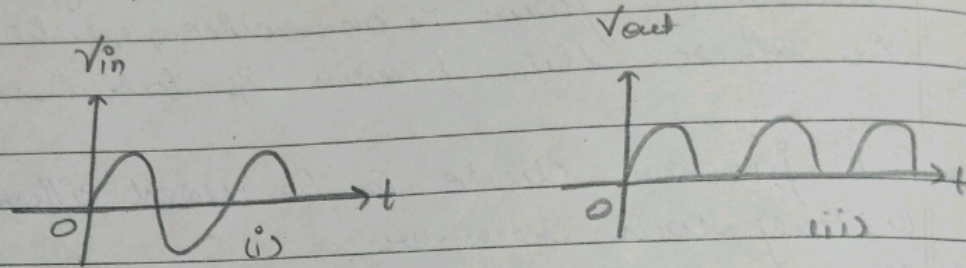End A is at +ve potential & Diode D is in R.O.B.,
 So, No current flows through load R_L &
 there is No output voltage across R_L



(we get output voltage as),

In the end. next +ve half cycle of AC input, we again get the output & so on.

◦ Since the rectified output of the circuit is obtained only for half of the input AC wave, the device is called half-wave rectifier.

◦ Advantages →

- (i) It is simple circuit
- (ii) low cost
- (iii) easy to use.
- (iv) easily construct
- (v) low No. of component, therefore it is cheap.


Disadvantages $\rightarrow$

- (i) transformer utilization factor is low.
- (ii) produce low output voltage.
- (iii) DC Saturation of transf. core resulting in $\rightarrow$ magnetizing current & also some hysteresis losses & generation of harmonics.
- (iv) Ripple factor is high & elaborate filtering is, therefore req. to give steady dc output.

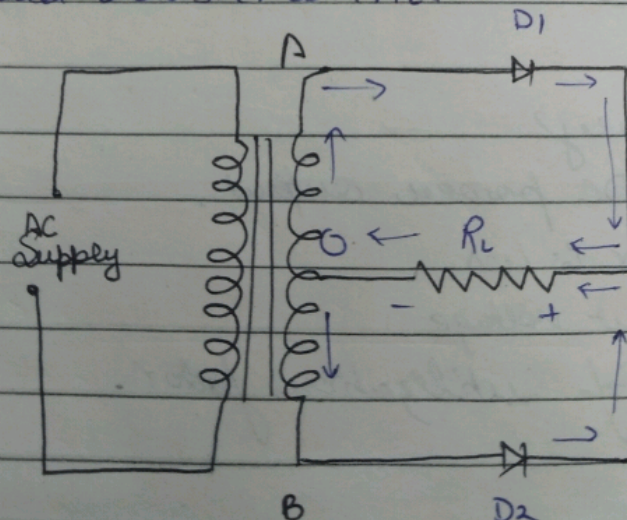(ii) Full wave Rectifier $\rightarrow$

A full wave rectifier is the rectifier which rectifies both halves of each AC input cycle & gives a unidirectional output voltage continuously.

Construction $\rightarrow$ In full wave rectifier, we use two semiconductor diode which operate in a complimentary mode. The AC input supply fed across primary coil P. The two ends A & B of the Secondary coil are connected to the p-ends of diode D_1 & D_2 resp. A load R_L is connected b/w both of the diodes. The DC output is obtained across the load resistance R_L .



(full wave rectifier).

working $\rightarrow$

During 1st half cycle of the Input Voltage $\rightarrow$


A terminal is +ve with respect to O while B terminal is -ve " " " O. Diode 1st is F.B & 2nd diode is R.B. & Does not conduct the current flow through R_L from D to O.

During 2nd half cycle $\rightarrow$

A is -ve and B is +ve w.r.t to O, thus diode 1st is R.B & 2nd diode is F.B.

The current flows through R_L in same dirⁿ.

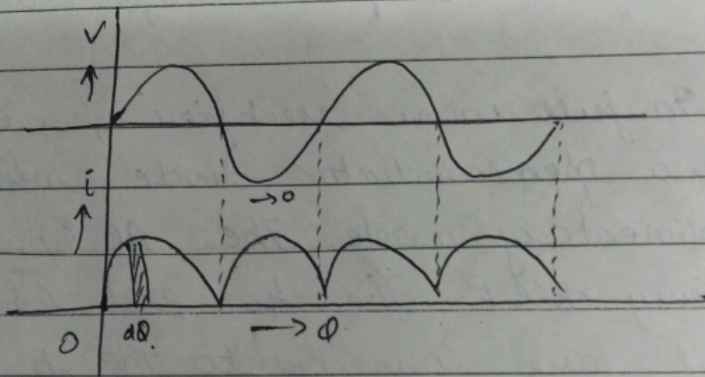The resulting output current is a continuous series.



• Advantages $\rightarrow$


- High Efficiency
- The large DC power output.
- Ripple factor is less
- Higher output voltage.
- Higher transf. utilization factor.

Disadvantages →

- More complicated than half wave rectifier.
- PIV rating of the diode is higher.
- The cost of the Centre tap of transf. is high.
- The rectifier is diff. to locate the Centre tap on the Secondary winding.
- It req. more diodes, two for Centre tap rectifier & four for bridge rectifier.


★ Zener diode → They are s/c devices that allow current to flow in both dirn but specialize in current flowing in reverse.

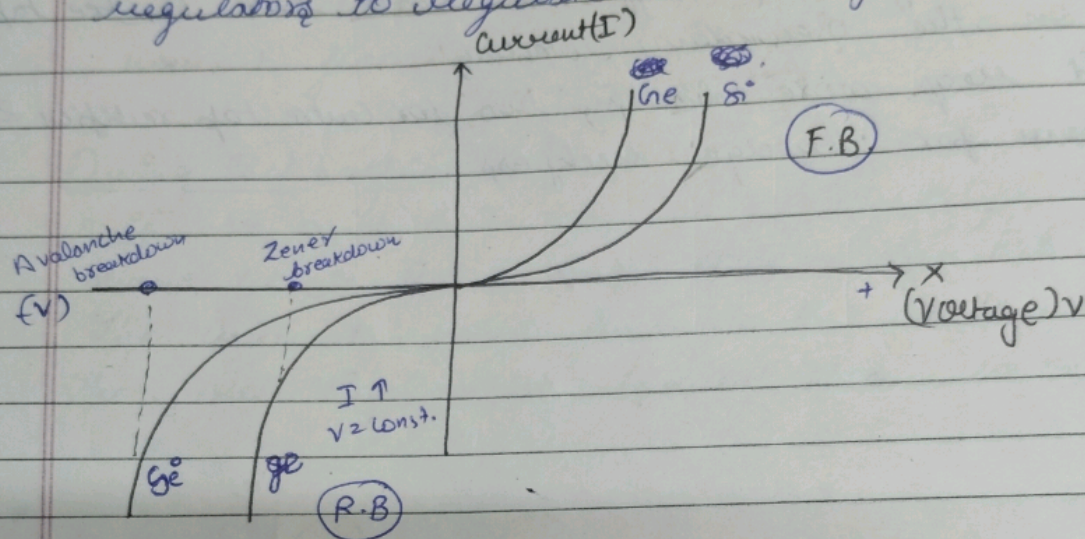- Also known as Breakdown diode.
- used as voltage references and as shunt regulators to regulate the voltage across small loads.




☞ Clamper Circuit → They are the electronic ckt. that shifts the DC level of the AC signal.


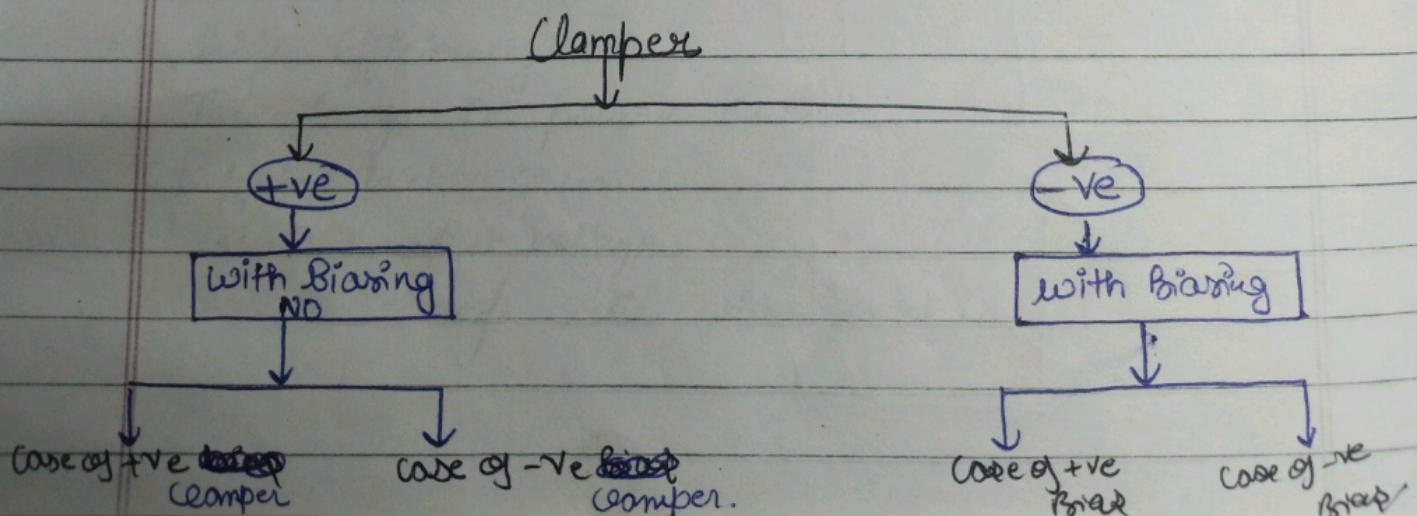
- Also known as DC Voltage restorers or level shifter.
- It is used to shift the waveform upward & downward.



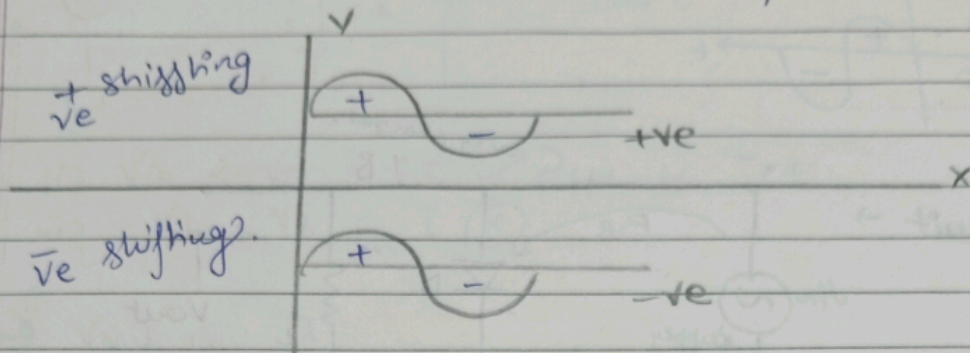
- The working of clamper circuit depend upon the -
Variation in the time constant of the capacitor.



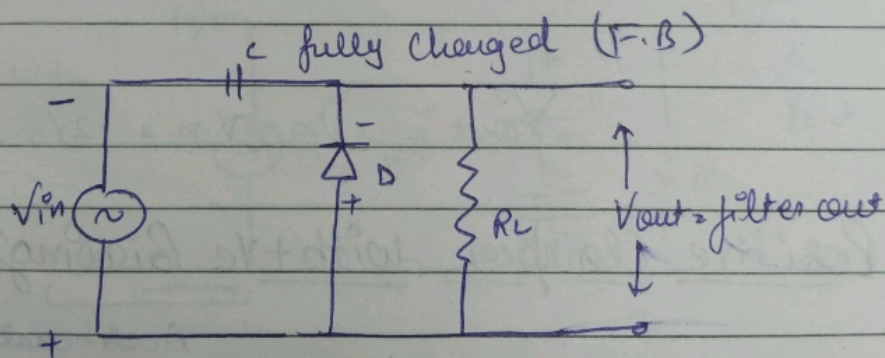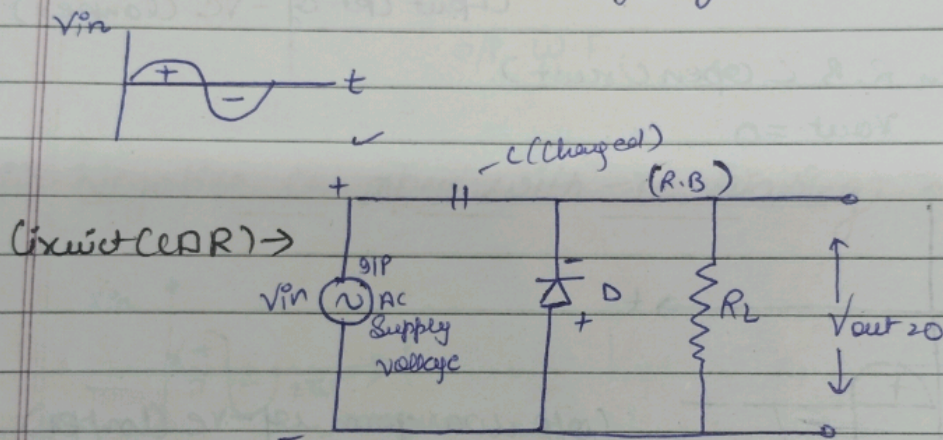- +ve Clamper $\rightarrow$ (+ve Shifting)




(+ve clamper.)

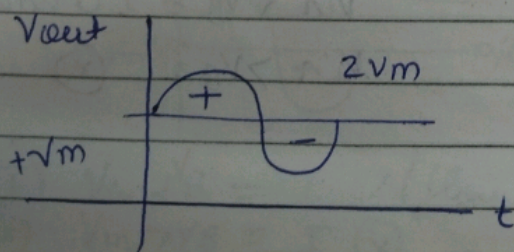



$V_{out} = V_m + V_m = 2V_m$

$\nearrow$ +ve cycle $\searrow$ -ve cycle

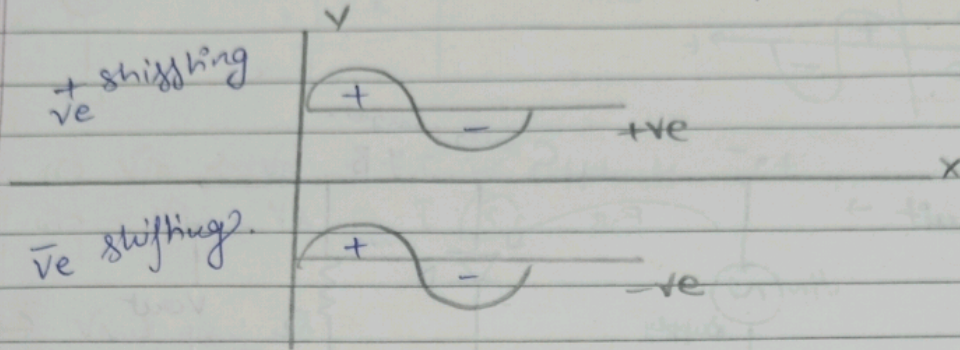
- The working of clamper circuit depend upon the -
Variation in the time constant of the capacitor.



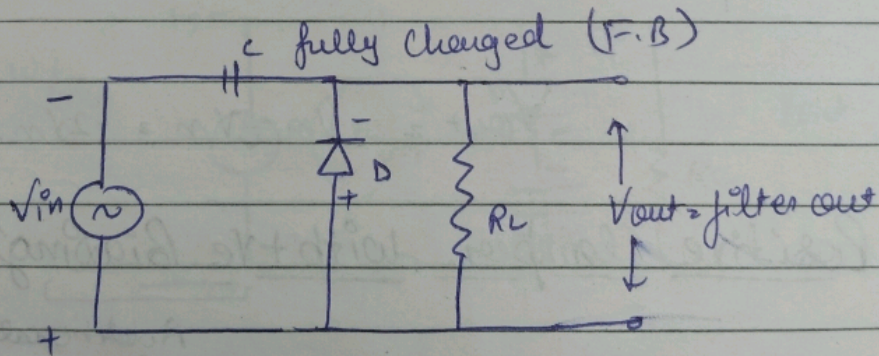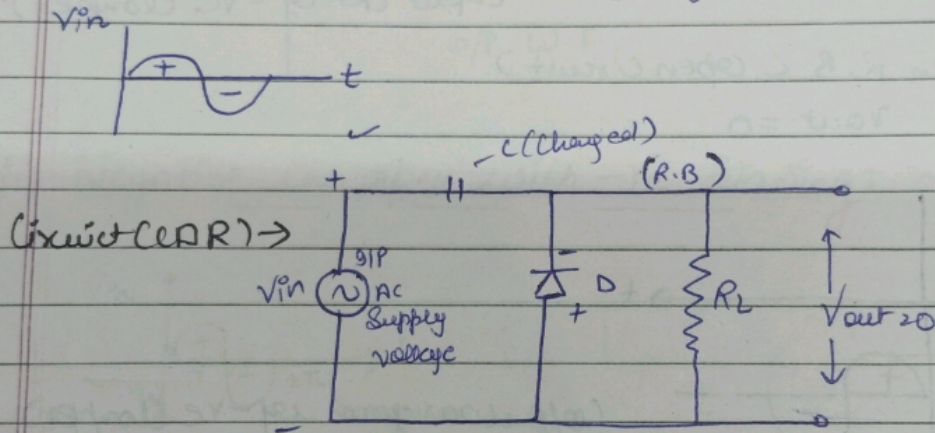- +ve Clamper $\rightarrow$ (+ve Shifting)





(+ve clamper.)

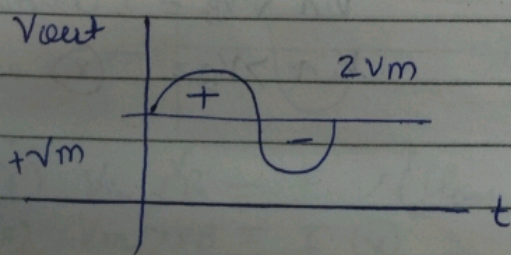


$$V_{out} = V_m + V_m = 2V_m$$
 (Note: V_m is the peak voltage of the input cycle, and V_m is the peak voltage of the capacitor during the second half-cycle.)

(2) -ve Clamper - (-ve shifting)

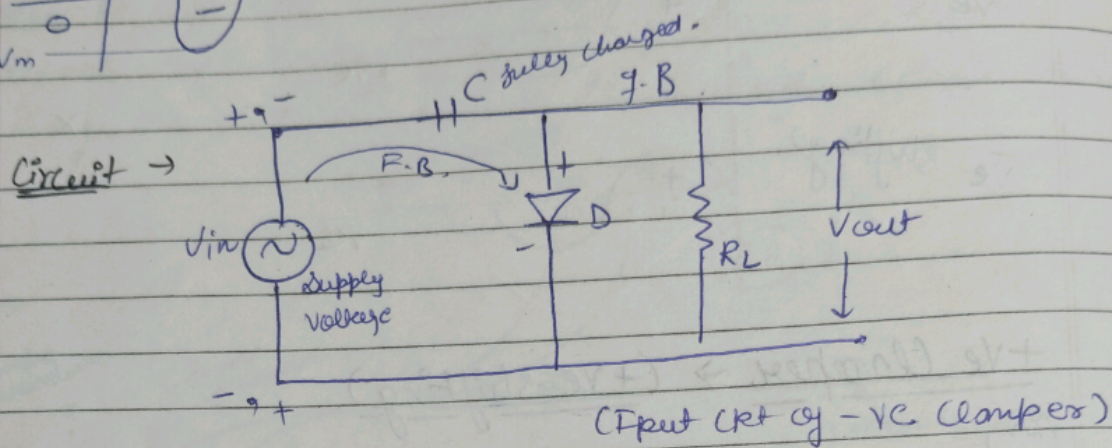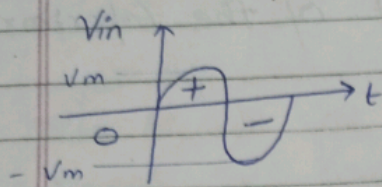

When R.B $\rightarrow$ open circuit.

$$V_{out} = 0$$


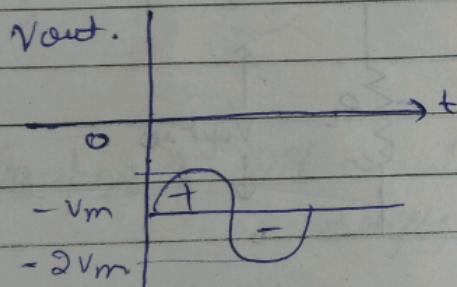


(O/P waveform of -ve clamper)

$$V_{out} = -V_m - V_m = -2V_m$$

* Positive Clamper with +ve Biasing $\rightarrow$


Additional shifting

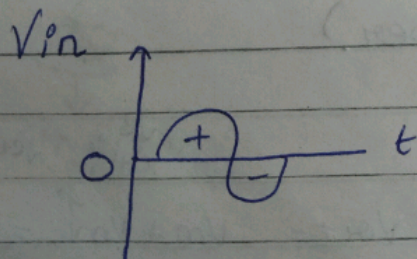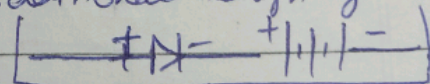


$$V_{in} < V_B \Rightarrow \text{Conducts}$$

$$V_{in} > V_B \Rightarrow \text{I} \otimes$$


Due to $V_{in} = D$ diode not conduct.

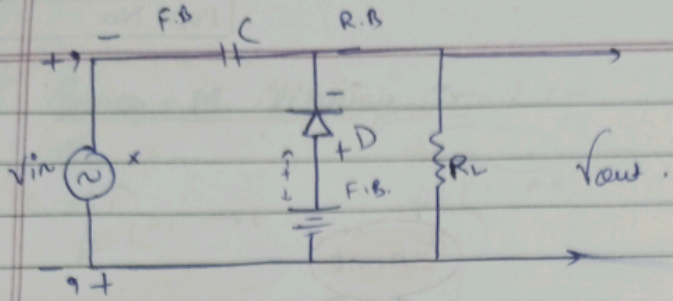


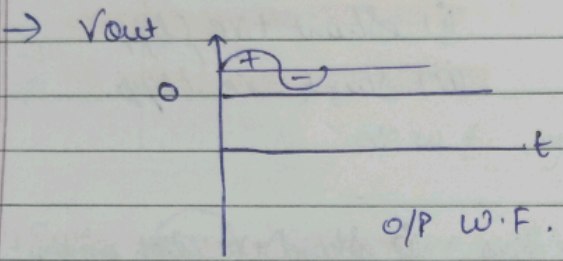
- (i) $V_{in} < V_B - I$ ✓ conducts.
- (ii) $V_{in} > V_B - I$ (X)



(ii) Negative clamper with -ve biasing →

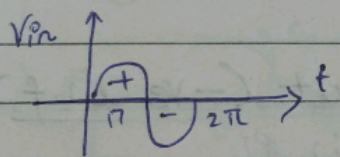


O/P W.F.

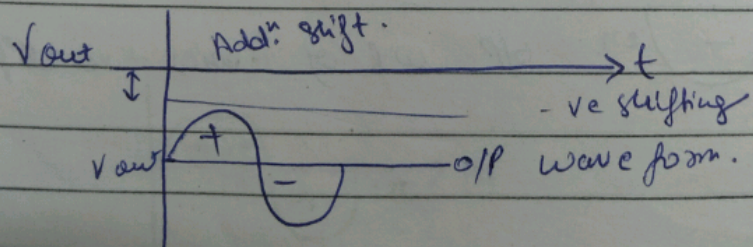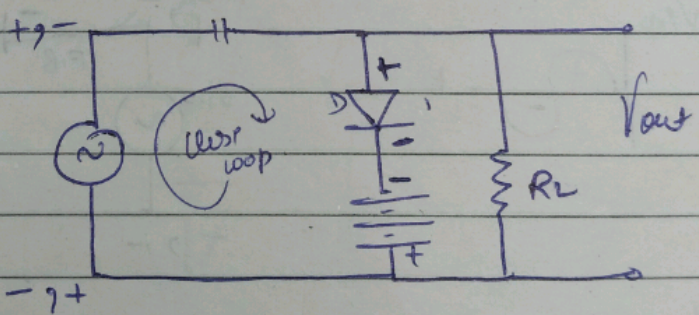

- (i) $V_{in} < V_B = I$ ✓ (flow)
- (ii) $V_{in} > V_B = I$ (X)

Clipping circuit $\rightarrow$

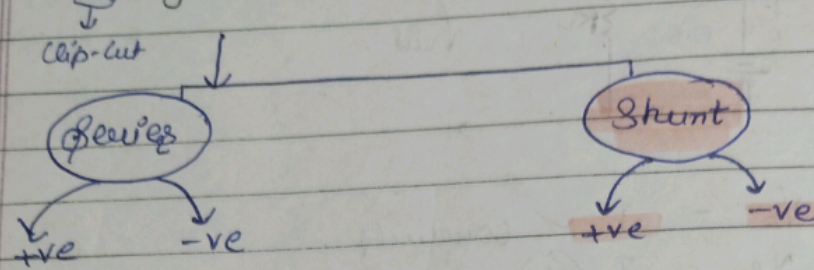

(A) Unbiased $\rightarrow$

- (i) Series +ve Clipping
- (ii) Series -ve Clipping

(i) Shunt +ve Clipp.

(ii) Shunt -ve Clipp.



(B) Biased $\rightarrow$

- (i) Series +ve Clipp with +ve Bias
- (ii) Series -ve Clipp with -ve Bias
- (i) Shunt +ve Clipp with +ve Bias
- (ii) Shunt -ve Clipp with -ve Bias.

(i) Series $\rightarrow$



(a) Series +ve Clipping Circuit (-ve w.f)

2 component (i) Diode (ii) R_L

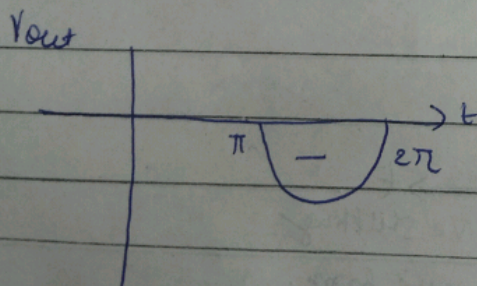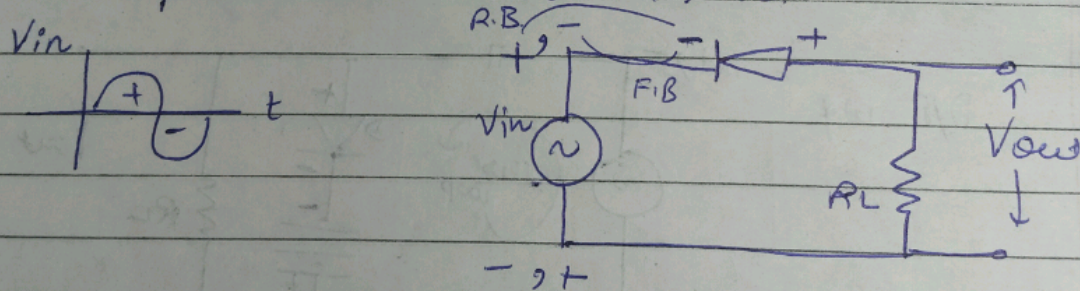

O/P w.f of Series +ve Clipping.

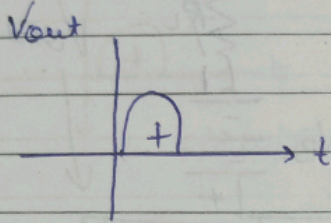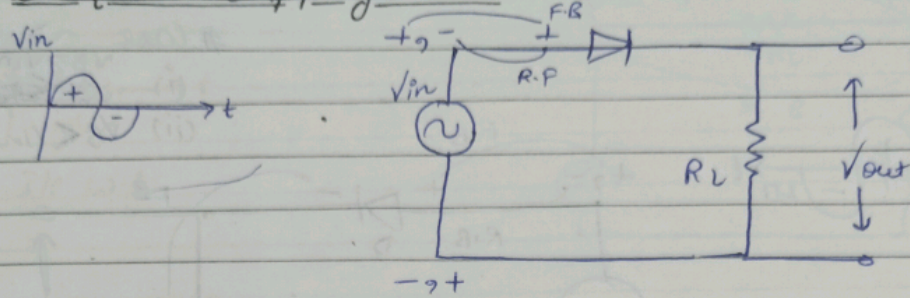(ii) Series -ve Clipping Circuit $\rightarrow$





o/p w.f. of -ve c.ckt. (Series).

(i) Series (+ve) Clipp. ckt. with +ve Biasing $\rightarrow$

Case $\rightarrow$

(i) $V_{in} < V_B$ - I flow



(ii) $V_{in} > V_B$ - I $\otimes$

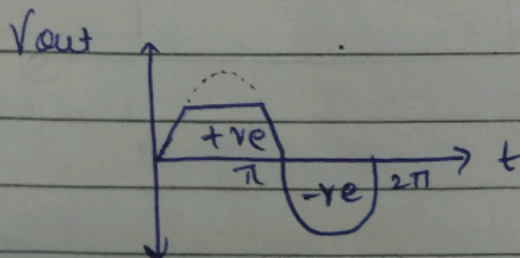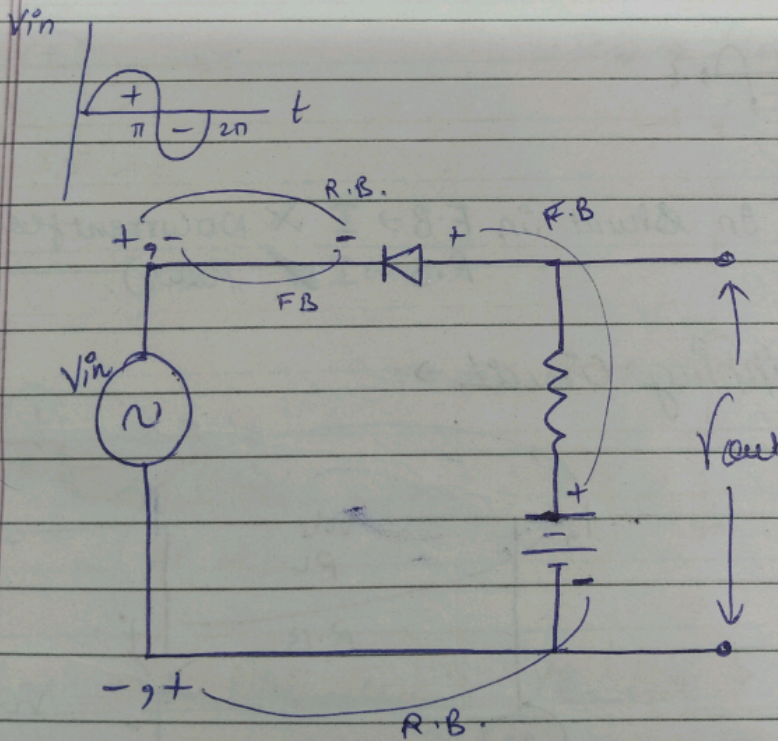

Q) Series -ve clipping with -ve bias $\rightarrow$



Case $\rightarrow$

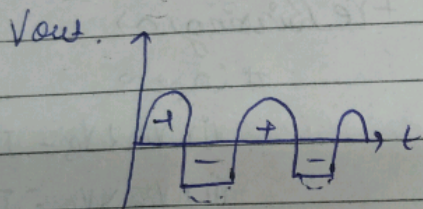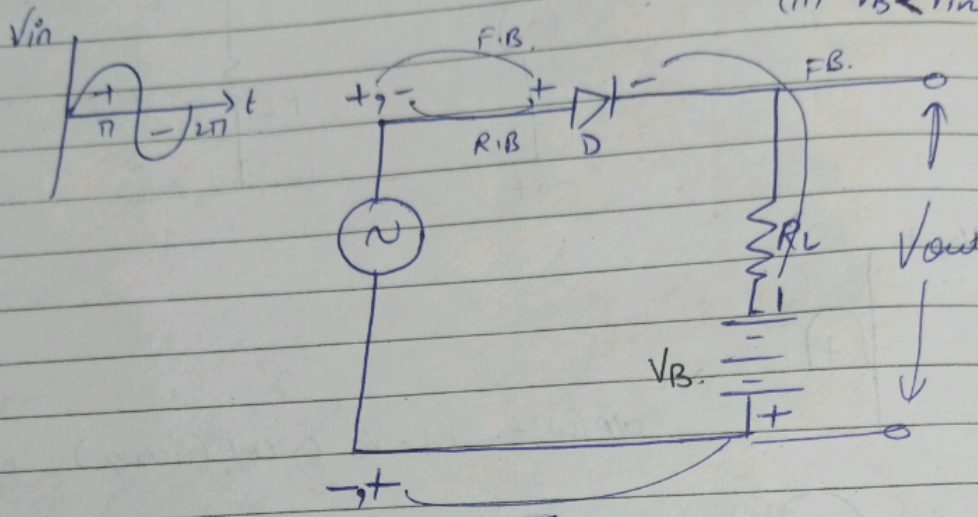- (i) ~~$V_B > V_{in}$~~ $- I \downarrow$
- (ii) $V_B < V_{in} = I \downarrow$ (X)






★ Shunt $\rightarrow$ (i) In Shunt in F.B $\rightarrow I \downarrow$ (No current flow)
 R.B $\rightarrow I \downarrow$ (flow).

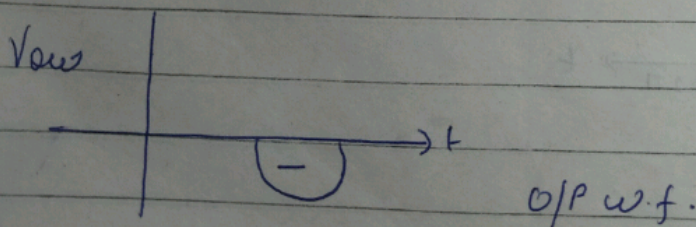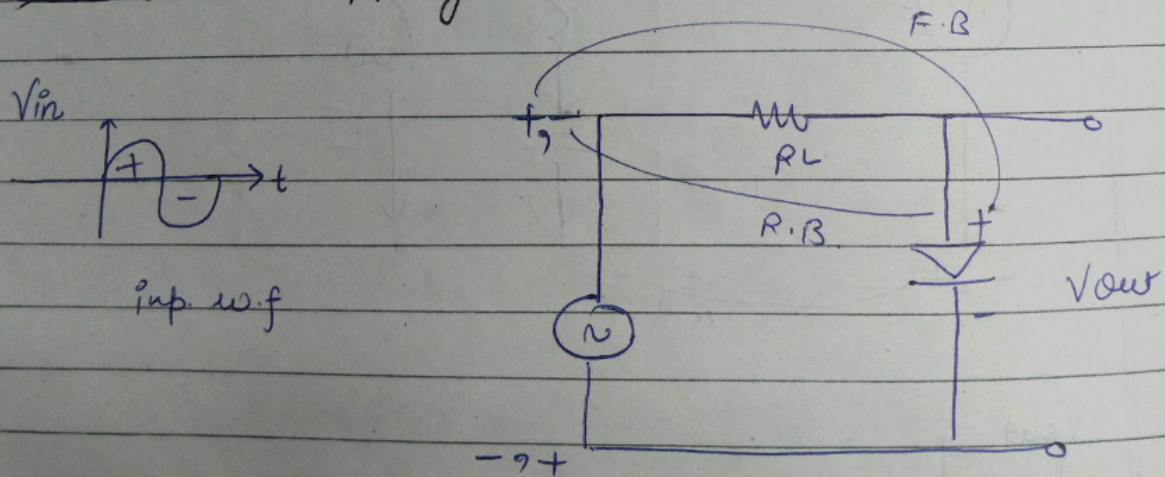(i) Shunt +ve Clipping Circuit $\rightarrow$




(ii) Shunt -ve Clipping cut →

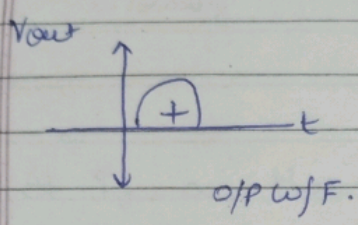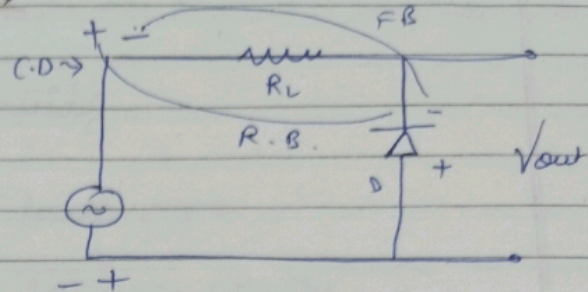
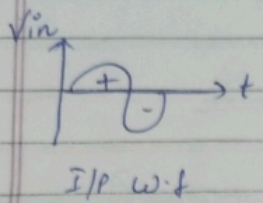


$$\begin{aligned} V_B > V_{in} - R_B I & \checkmark \\ V_B < V_{in} - R_B I & \times \end{aligned}$$

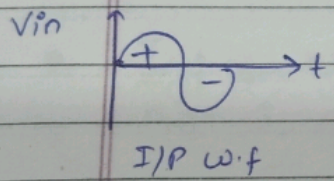(a) Shunt +ve Clipping with +ve biasing →



C.D. → Circuit diag. →

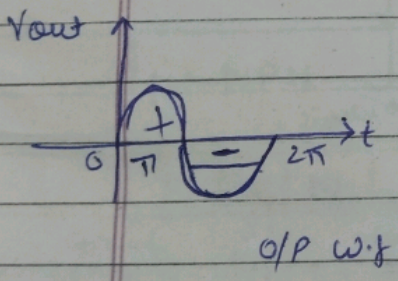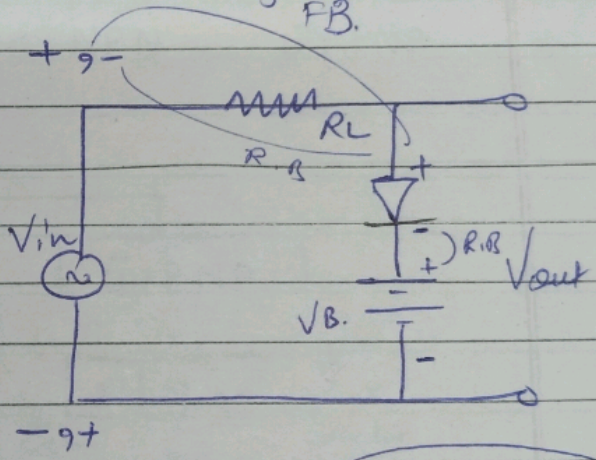

$$\begin{aligned} V_{in} > V_B - I R_B & \checkmark \\ V_{in} < V_B - I R_B & \times \end{aligned}$$

(b) Shunt -ve clipp. with -ve bias →

Circuit Diag. - (CD) →

