 


Decoders and Encoders


Decoder is a combinational circuit that converts n lines of input to 2^n lines of output. It is a multiple input and multiple output device.

Input - n
Output - 2^n



- Applications of decoder are - $n \times 2^n$
- i) Binary to octal - 3×8
 - ii) Binary to Hexadecimal - 4×16
 - iii) Binary to decimal - 4×10

Ex- If we have to design 3×8 decoder

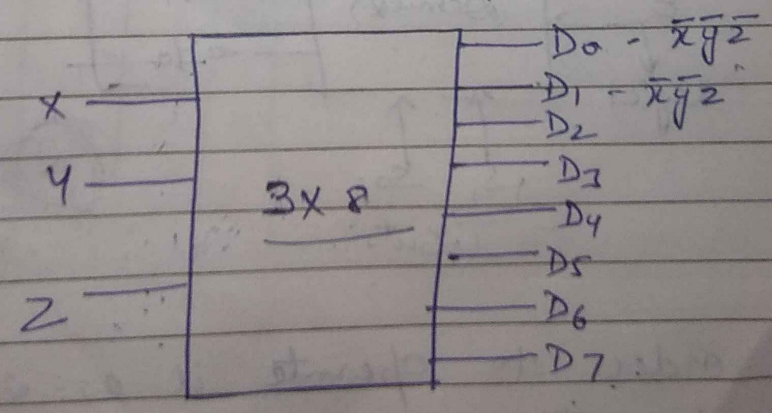


$2^n \rightarrow 16$
 $n \rightarrow 4$

Truth Table

x	y	z	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	1	0
0	1	0					1	1		
0	1	1					1			
1	0	0				1				
1	0	1			1					
1	1	0	1							
1	1	1	1							


Demultiplexer as Decoders

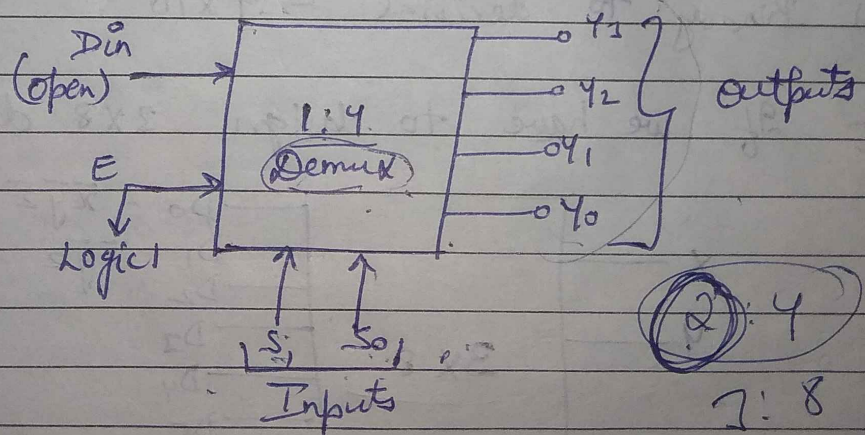- We can use a demultiplexer as a decoder.
- We will be using 1:4 Demux as 2:4 decoder.



→ In order to operate it as 2:4 decoder, we have to use S_1, S_0 as inputs, keep D_{in} open and use Y_3 to Y_0 as outputs.


BCD to Seven - Segment Display

 

LED display

D.N.	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	1	1					
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0							
9	1	0	0	1							

Priority Encoders

 

→ This is a special type of Encoder

→ Priorities are given to the input lines.

If two or more input lines are '1' at the same time, then the input line with highest priority will be considered.

→ We assume that D_0 have the lowest priority and D_3 have the highest priority

Truth Table

D_3	D_2	D_1	D_0	A	B
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1


Parity Generator

- 0 0 → I_0
- 0 1 → I_1
- 1 0 → I_2 ✓
- 1 1 → I_3

Parity Generator

We already know about


- Even Parity
- Odd Parity

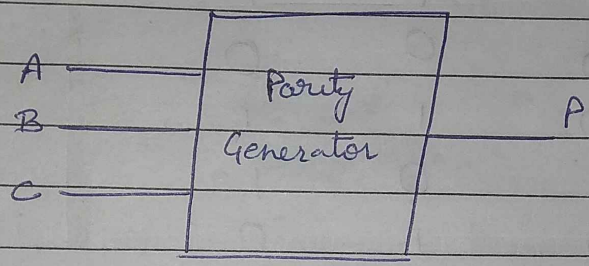

Even Parity Generator

A	B	C	P
0	0	0	0
0	0	1	1 ✓
0	1	0	1 ✓
0	1	1	0
1	0	0	1 ✓
1	0	1	0
1	1	0	0
1	1	1	1 ✓

 
$$\begin{aligned}
 P &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\
 &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\
 P &= A \oplus B \oplus C
 \end{aligned}$$




Odd - Parity Generator

A	B	C	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$P = \overline{A \oplus B \oplus C}$$

 


Block Diagram

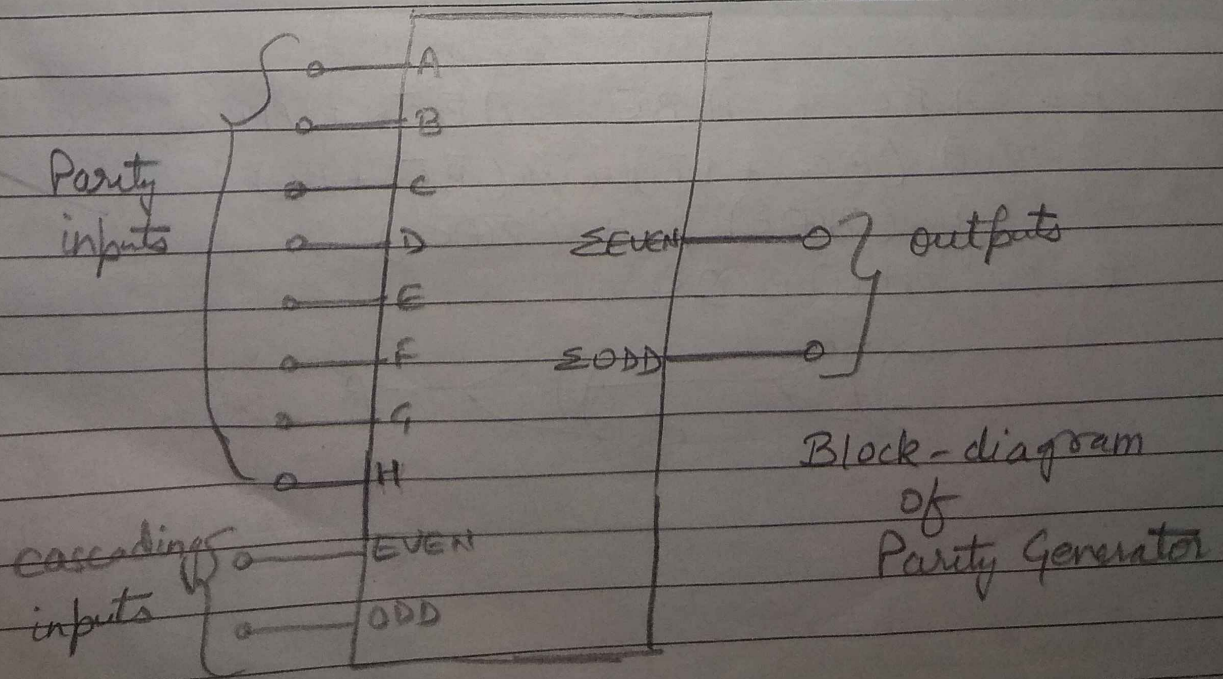

Digital comparators

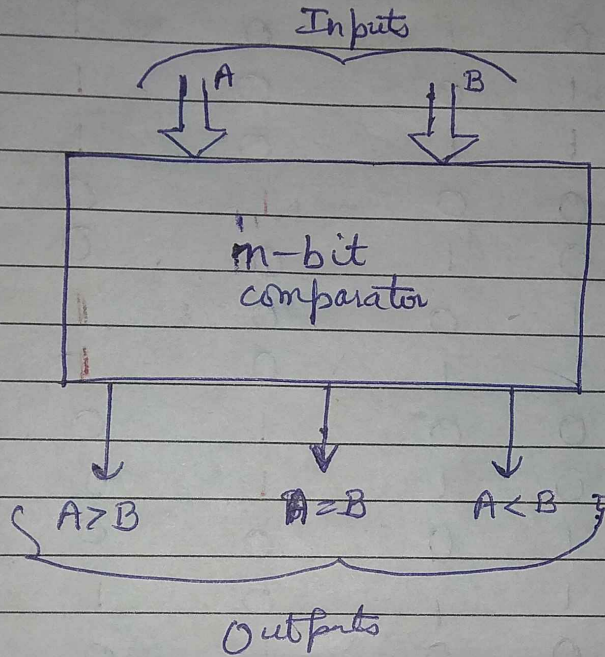Comparators can be designed for comparing multibit numbers:




A	B	Y
0	0	A = B
0	1	A < B
1	0	A > B
1	1	A = B

$A < B = \bar{A}B$
 $A = B = \bar{A}\bar{B} + AB$
 $A > B = A\bar{B}$

Now, a 2-bit digital comparator

A, A₀ → 00, 01, 10, 11

B, B₀ → 00, 01, 10, 11

 

P.T.O

Truth Table of 2-bit comparator


A_1	A_0	B_1	B_0	$A > B$	$A < B$	$A = B$
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

Thus, for a n -bit comparator —
We have

$2n$ variables
and 2^{2n} rows

For,
 
$$\underline{A = B} = (A_1 \odot B_1) (A_0 \odot B_0)$$



For $A > B$ $\Rightarrow A_1 > B_1$ or
if $A_1 = B_1$ and $A_0 > B_0$

Case 1 $A = 10$
 $B = 01$

Case 2: $A = 10$
 $B = 10$

For $A < B$ $\Rightarrow A_1 < B_1$ or
if $A_1 = B_1$ and $A_0 < B_0$

Case 1
 $A = 01$
 $B = 11$

Case 2
 $A = 10$
 $B = 11$

Code Converters

There is a wide variety of binary codes used in digital systems such as BCD, excess-3, gray, octal, hexadecimal etc.

Often it is required to convert from one code to another.

Ex - 4 bit binary \longrightarrow BCD conversion

TRUTH-TABLE

Binary No.				Decimal	BCD				
B ₃	B ₂	B ₁	B ₀		D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	0	0	1
0	0	1	0	2	0	0	0	1	0
0	0	1	1	3	0	0	0	1	1
0	1	0	0	4	0	0	1	0	0
0	1	0	1	5	0	0	1	0	1
0	1	1	0	6	0	0	1	1	0
0	1	1	1	7	0	0	1	1	1
1	0	0	0	8	0	1	0	0	0
1	0	0	1	9	0	1	0	0	1
1	0	1	0	10	1	0	0	0	0
1	0	1	1	11	1	0	0	0	1
1	1	0	0	12	1	0	0	1	0
1	1	0	1	13	1	0	0	1	1
1	1	1	0	14	1	0	1	0	0
1	1	1	1	15	1	0	1	0	1

Boolean Equation - Solving for D_0, D_1, D_2, D_3 & D_4
 by using K-Map -

$$D_0 = B_0$$


$$D_1 = B_3 B_2 \bar{B}_1 + B_3 B_1$$

$$D_2 = \bar{B}_3 B_2 + B_2 B_1$$

$$D_3 = B_3 \bar{B}_2 \bar{B}_1$$

$$D_4 = B_3 B_2 + B_3 B_1$$

Circuit diagram

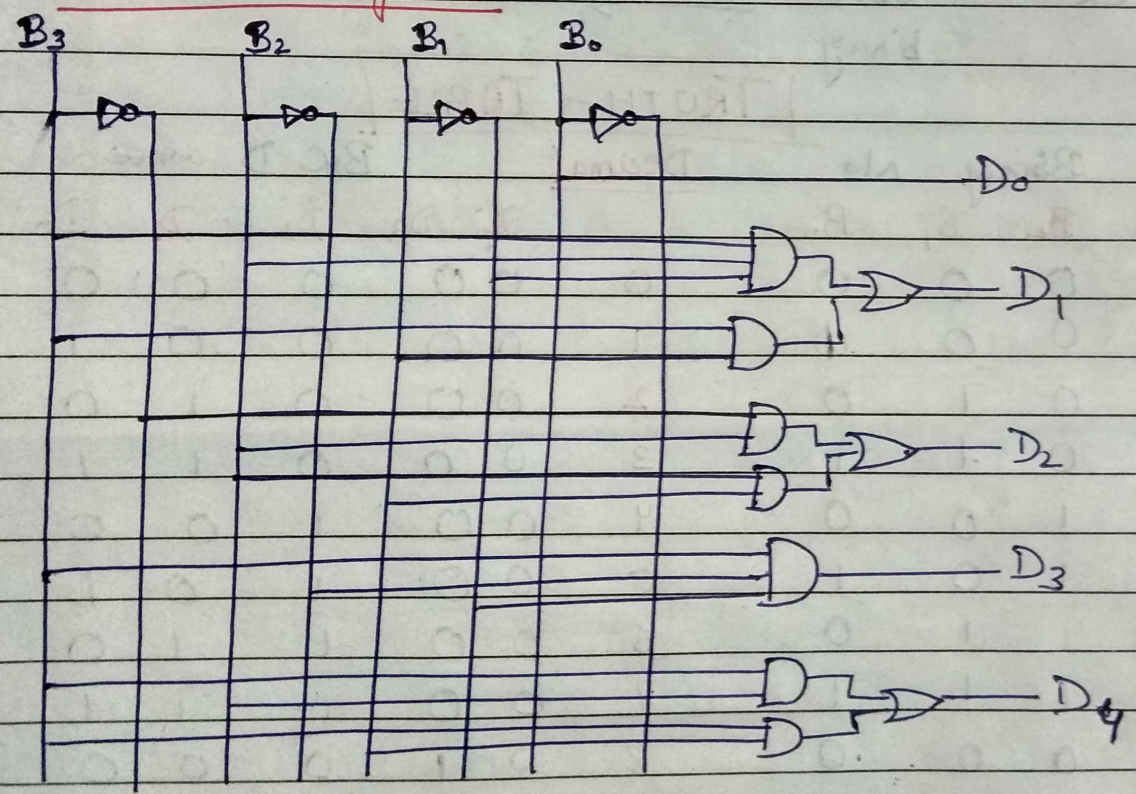


BCD Arithmetic

i) BCD Addition

- BCD adder adds two BCD digits and produces a BCD digit.
- But, a BCD digit can't be greater than 9.
- If sum is less than or equal to 9 and carry = 0, then no correction is necessary. The sum obtained is correct and in the true BCD form.
- But if sum is invalid BCD or carry = 1, then result is wrong and needs correction.
- The wrong result can be corrected by adding six i.e. (0110) to it.

Block Diagram of BCD Adder

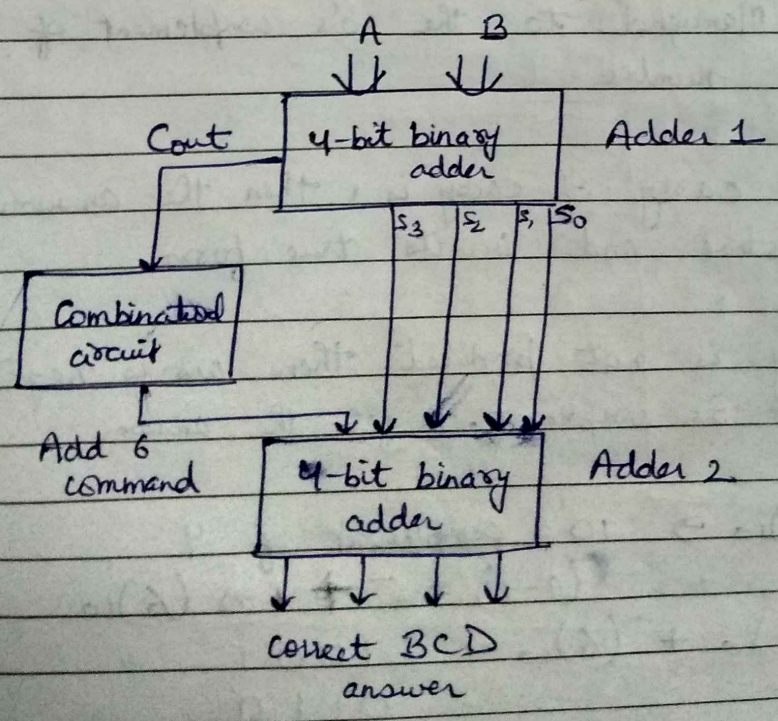

ii) BCD Subtractor

BCD subtraction can be performed using 2 methods -

- i) Using 9's complement
- ii) Using 10's complement

→ 9's complement of a BCD number is given by 9 minus that number

Ex -

$$\begin{aligned} 9's \text{ complement of } 7 &\rightarrow 0111 \text{ is} \\ 9-7=2 &\Rightarrow \underline{0010} \end{aligned}$$

→ 10's complement of a BCD no.

\Rightarrow 9's complement of the number + 1

BCD Subtraction using 10's complement

Step 1 → Obtain the 10's complement of 'number to be subtracted'.

Step 2 → Add Minuend to the 10's complement of the number.

Step 3 → Discard carry. If carry is 1 then the answer is positive and in its true form.

Step 4 → If carry is not produced then ans. is negative. So, take 10's complement to get the answer.

Ex - $(9)_{10} - (4)_{10} \rightarrow$ 10's complement of 4


$$\Rightarrow (9-4) = 5 + 1 \Rightarrow (6)_{10}$$

$$\rightarrow (9)_{10} + (6)_{10} \Rightarrow \begin{array}{r} 1001 \\ 0110 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} 0110 \\ 1111 \\ \hline 1111 \end{array} \leftarrow \text{Invalid BCD} \\ \text{ \& carry } 20$$

Add $(0110)_{10}$ for correction

Adding $(0110)_{10}$ for correction

 

Discard the carry

Answer is $(5)_{10}$


Arithmetic Logic Unit (ALU)

→ ALU is a combinational circuit which performs arithmetic and logical operation.

→ Arithmetic operation includes - Addition, Subtraction, increment, decrement etc.

Logical operation - NOT, NAND, OR, AND, NOR, XOR

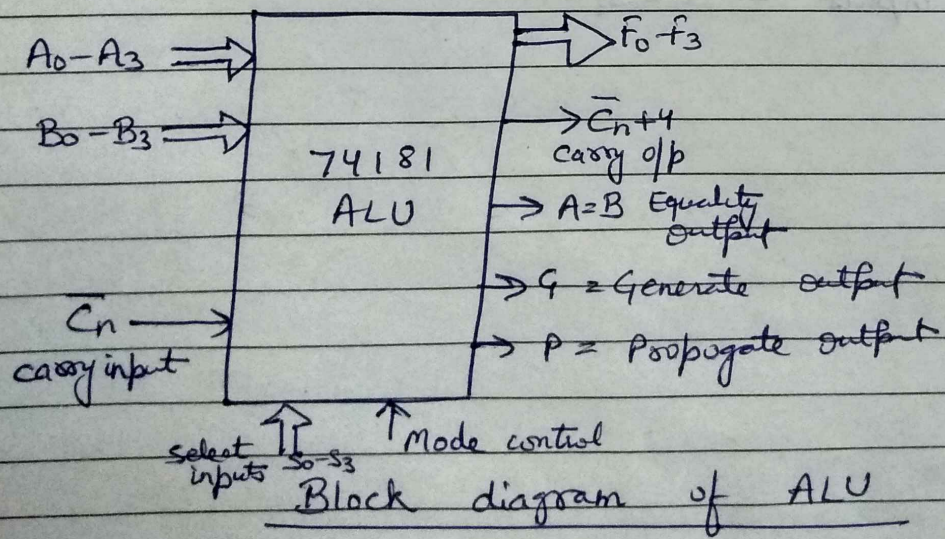→ ALU is the most important part of processor.



→ A_0-A_3 and B_0-B_3 are the two 4-bit numbers as inputs

→ $\bar{C}_n \rightarrow$ carry input

If $\bar{C}_n = 1$ means there is no carry.

$\bar{C}_n = 0$ means there is carry

Page	
Date	

→ $F_0 - F_3 \Rightarrow$ 4-bit o/p data

→ $\bar{C}_{n+4} \rightarrow$ Carry o/p

If we do the addition and we get one extra bit as o/p, then that bit will be shown over here.

→ $A=B$ Equality o/p

If $A=B$, then Equality o/p = 1

→ G and P pins are used for cascade mode. These pins are used when 2 or more ALUs are used.

→ Mode control, M

$M=0 \rightarrow$ arithmetic operation

$M=1 \rightarrow$ Logical operation

→ Select inputs - $S_0 - S_3$


Carry Look Ahead Adder

→ In parallel adders, where n adders are connected in sequence to add the numbers, the carry out of the previous stage is connected to carry in of the next stage.

→ The carry is said to be propagated like ripple, this phenomenon is called ripple carry propagation.

→ Due to this ripple carry propagation time delay is introduced in the addition process. This time delay is called as the propagation delay.

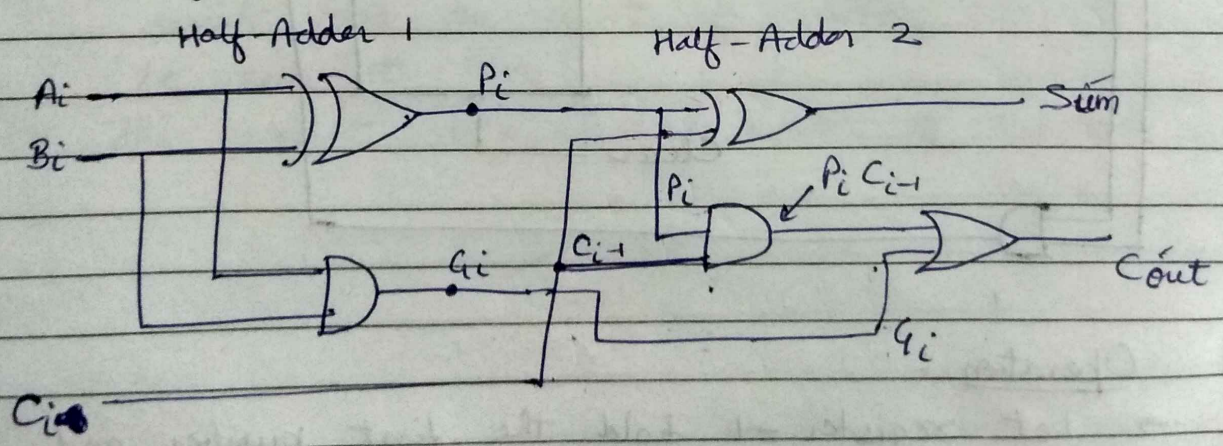→ The problem of propagation delay can be eliminated by using this addition technique of carry look-ahead adder.




$$P_i = A \oplus B$$

$$G_i = AB$$

$S = P_i \oplus C_i$ $C_{out} = G_i + P_i C$
--

Serial Adder

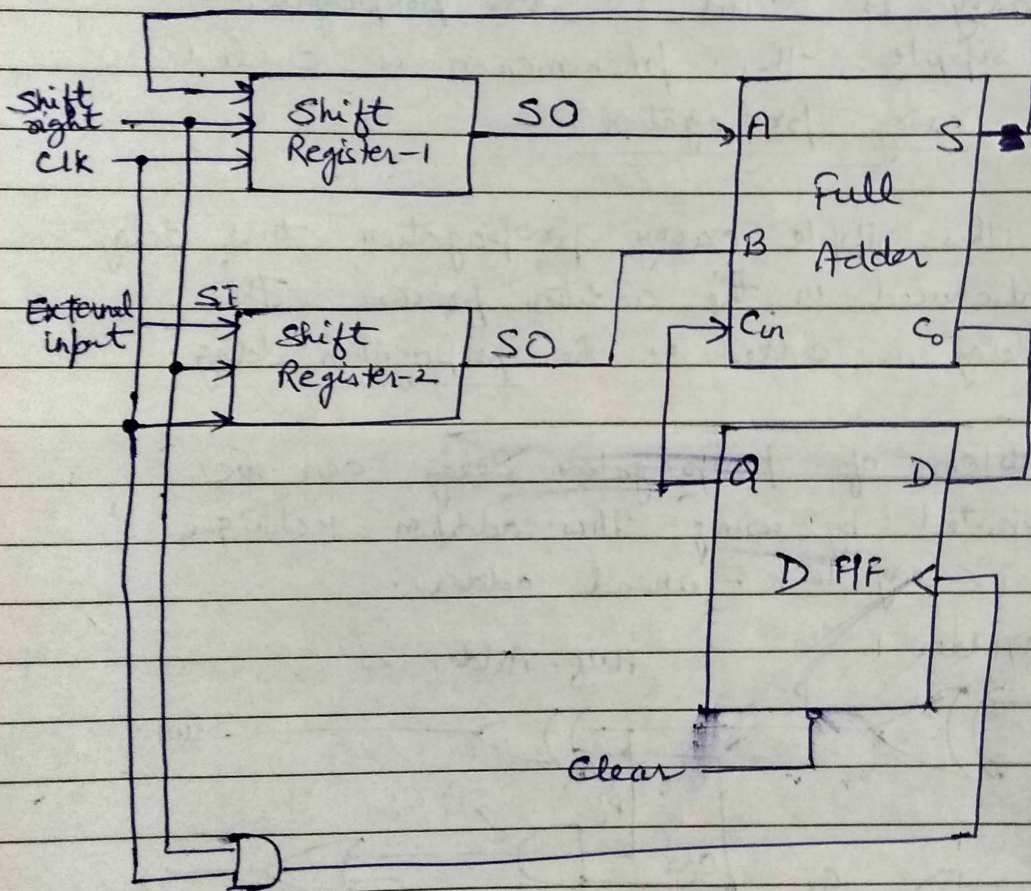- Serial Adder is used to add two n -bit numbers.
- Unlike the parallel adder, its speed is slow & it requires ~~less~~ ^{more components} equipments.
- It is a sequential circuit means ~~the~~ it is memory-based.



Operation :

- Let register-1 hold the first number and register-2 hold the other number.
- The D flip-flop is cleared initially so $Q=0$ and $C_{in}=0$

- The serial outputs (SO) of the two registers will provide the LSBs of the two numbers. They will act as bits A and B for the full adder.
- Full Adder will add these bits & produce sum S and carry out C_0 .
- Now, a clock pulse is applied to both the shift registers. So, the two numbers are right shifted by one bit each.
- The same operation will continue and we will get the addition of two numbers in a bit by bit manner.

Disadvantages of Serial Adder

- i) More time is required to complete the addition
- ii) A complicated circuit is required.
- iii) The sum & carry are available in the serial form so result of addition cannot be seen at once.
- iv) The circuit contains more number of components.